

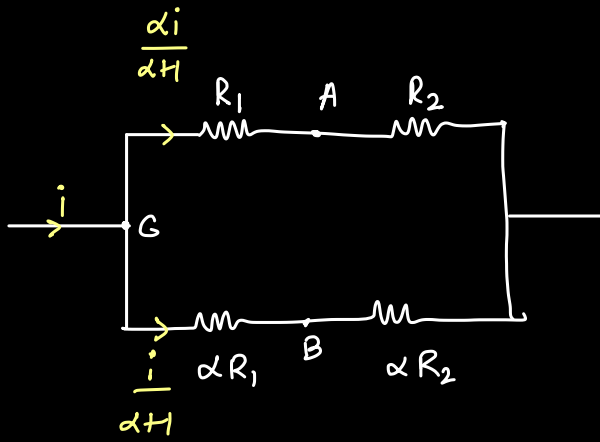


Wheatstone bridge

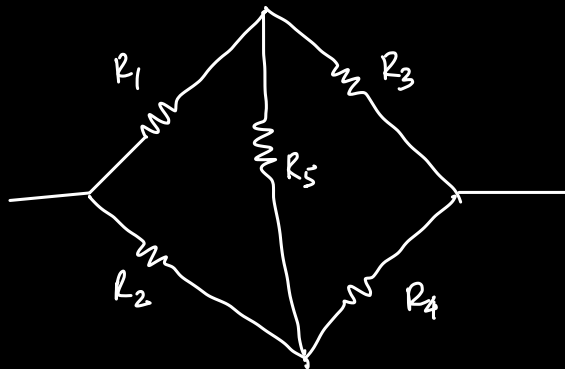



$$\left. \begin{aligned} V_C - V_A &= \frac{\alpha i}{\alpha t} \cdot R_1 \\ V_C - V_B &= \frac{i}{\alpha t} \cdot \alpha R_1 \end{aligned} \right\}$$

$$V_A = V_B$$

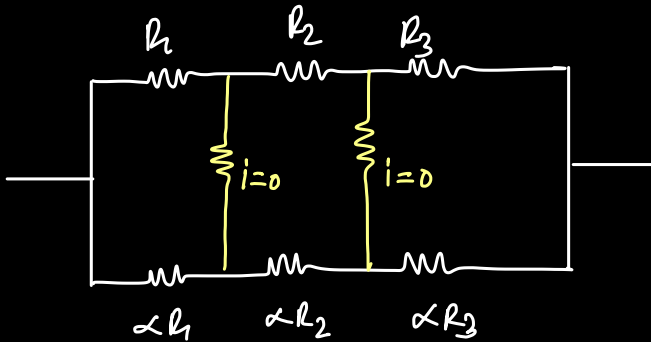


If $\frac{R_1}{R_2} = \frac{R_3}{R_4} \Rightarrow$ no current through R_5

It can be removed from circuit

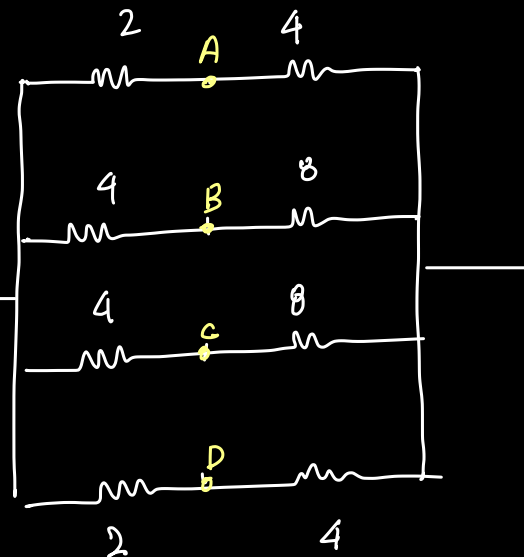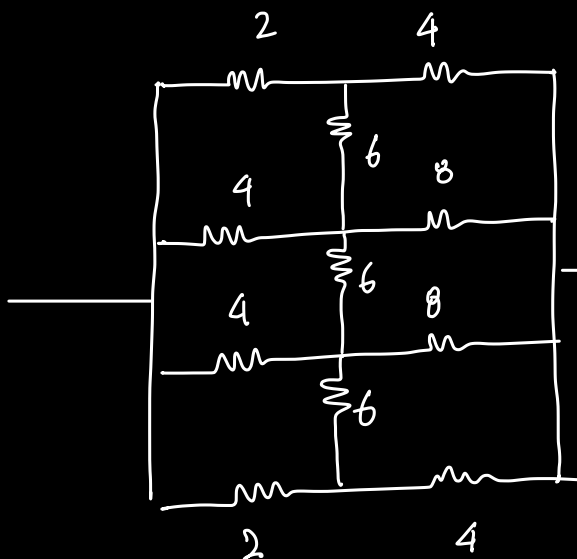


without 6Ω resistances
 $V_A = V_B = V_C = V_D$

Problems related to symmetric circuits

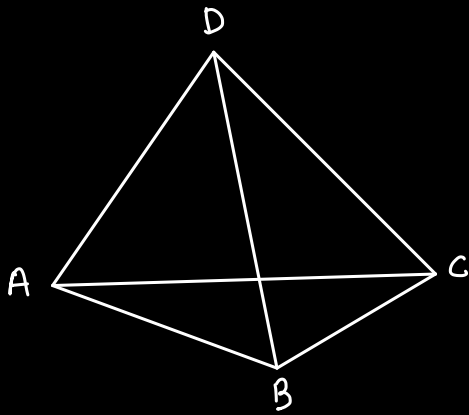

Find equivalent resistance between A & B

method 1

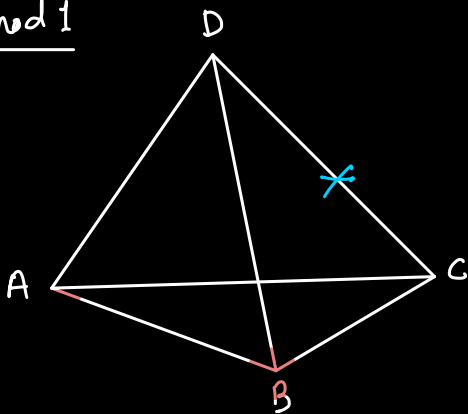

method of equipotential points

path of A is identical for C & D



path of B is identical for C & D

$$V_C = V_D$$

P & Q are equipotential if path to A is same for both P & Q. And path to B is same for both P & Q


method 2:

flatten 2D $\rightarrow$ 3D & observe symmetry

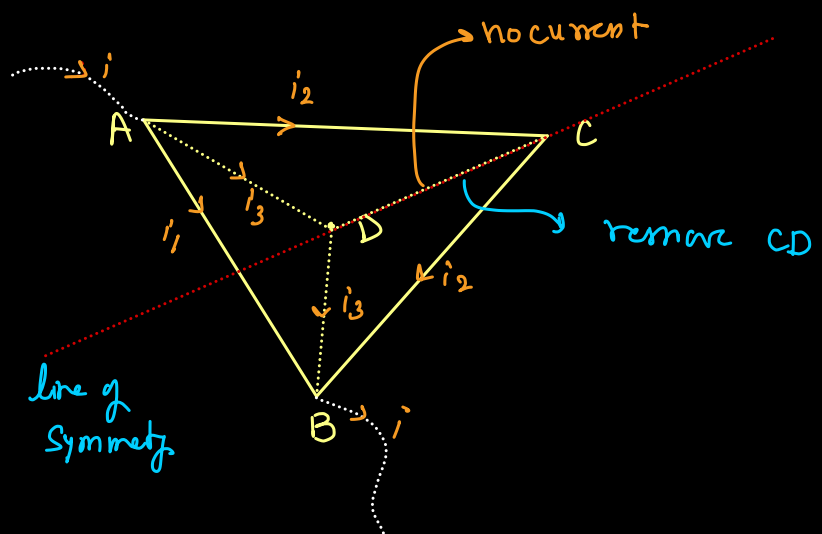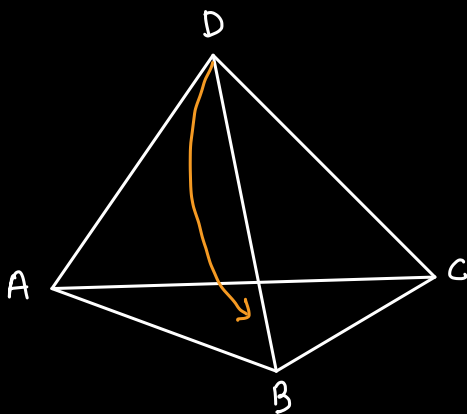


method 3

method of superposition


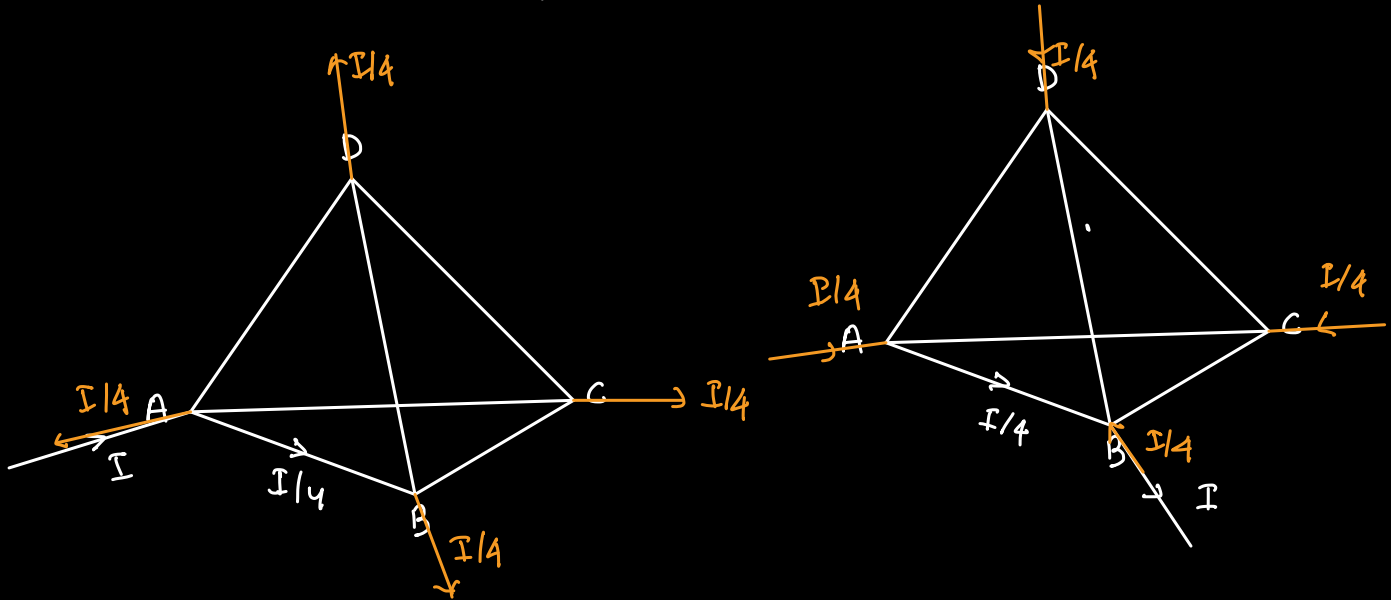


on superposition

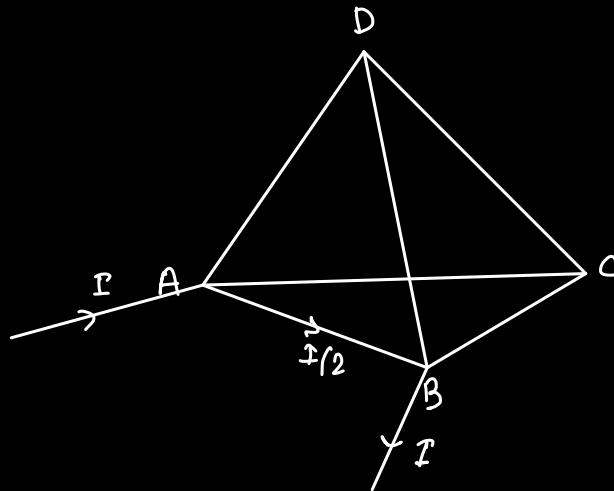


$$\Delta V_{AB} = IR_{eq} = I/2 R \Rightarrow R_{eq} = \frac{R}{2}$$

Ex.

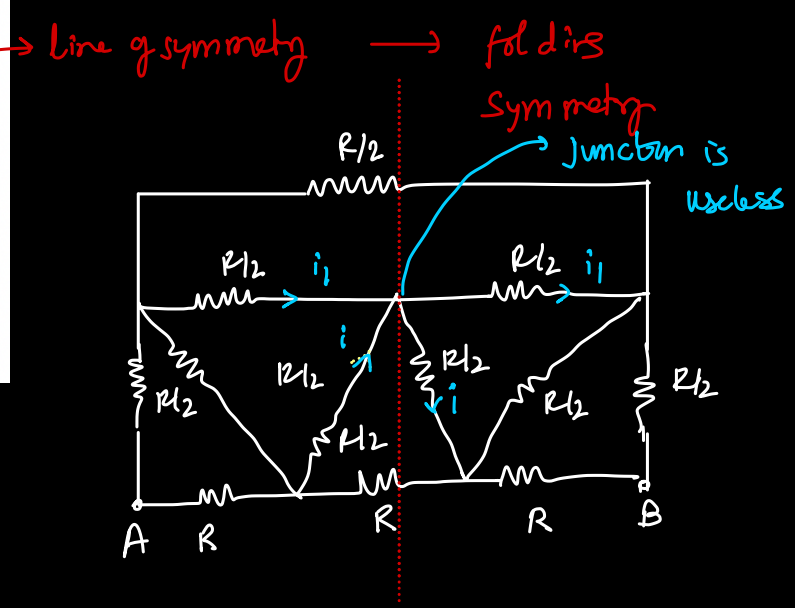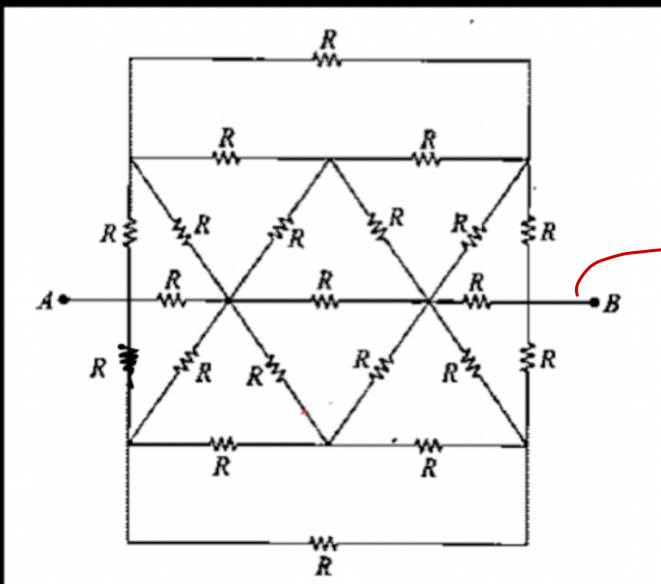


Junction can be detached

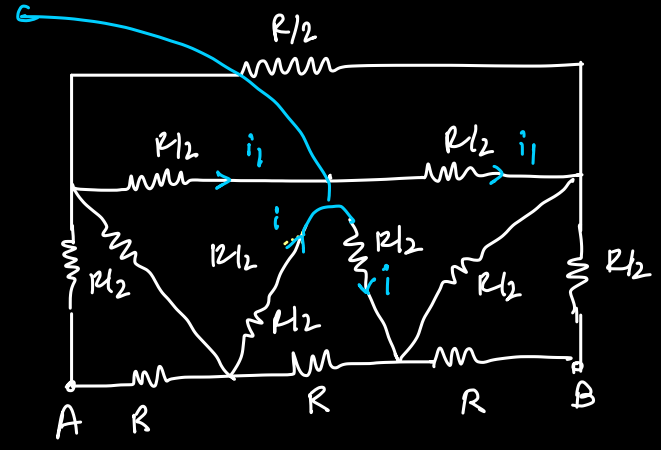

What do we want

$$2V = iR = i(KR)$$

→ equivalent resistor

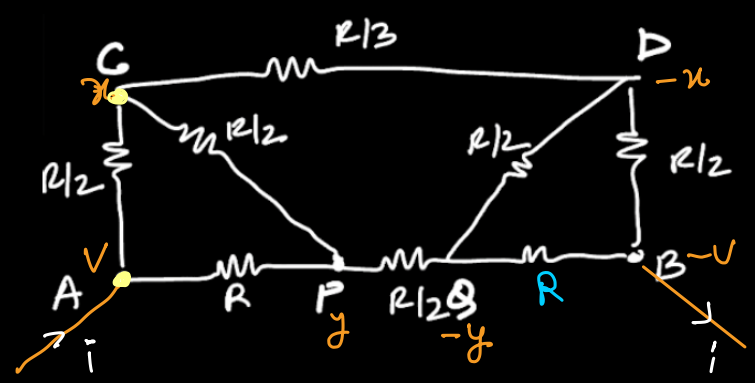

$$i = \frac{V-x}{R/2} + \frac{V-y}{R}$$

At C




$$\frac{x-V}{R/2} + \frac{x-y}{R/2} + \frac{2x}{R/3} = 0$$

Solve for x & y

At P

$$\frac{y-V}{R} + \frac{y-x}{R/2} + \frac{2y}{R/2} = 0$$

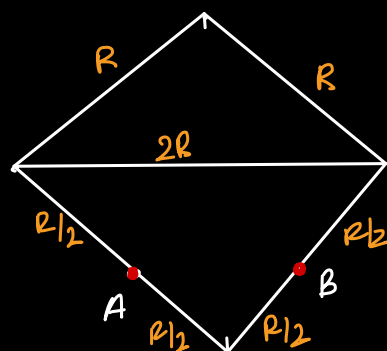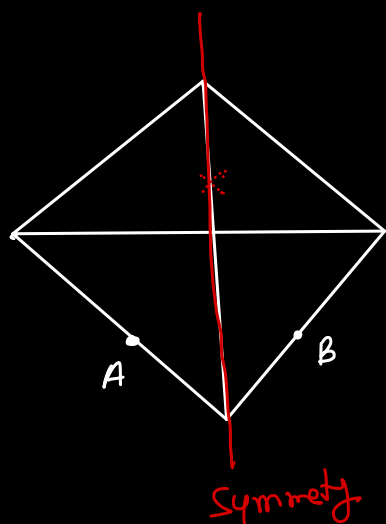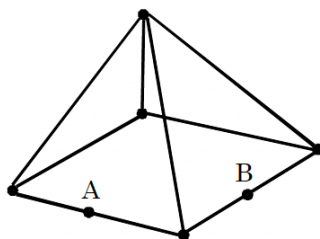A regular pyramid of square is made of eight identical wires each resistance $12\ \Omega$ shown in the figure. The terminals A and B are the mid-points of the corresponding sides. Find equivalent resistance between the terminals A and B in ohms.




$$R_{AB} = 8\ \Omega$$

HW

Paragraph for Questions no. 12 to 14

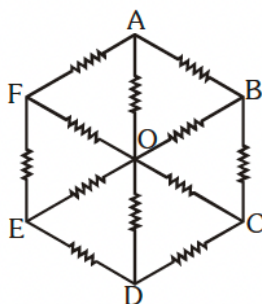Twelve wires of equal resistance R are placed in a given arrangement as shown in figure. Then find



2. Equivalent resistance between A & B is

- (A) $\frac{11R}{20}$ (B) $\frac{10R}{20}$ (C) $\frac{R}{20}$ (D) $\frac{3R}{2}$












3. Equivalent resistance between A & C is

- (A) $\frac{3R}{4}$ (B) $\frac{R}{4}$ (C) $\frac{5R}{6}$ (D) $\frac{3R}{5}$

4. Equivalent resistance between A & O is

- (A) $\frac{19R}{41}$ (B) $\frac{20R}{41}$ (C) $\frac{18R}{23}$ (D) $\frac{9R}{20}$





Resistance cubes

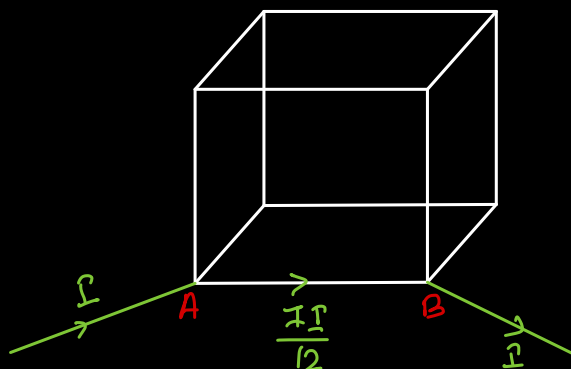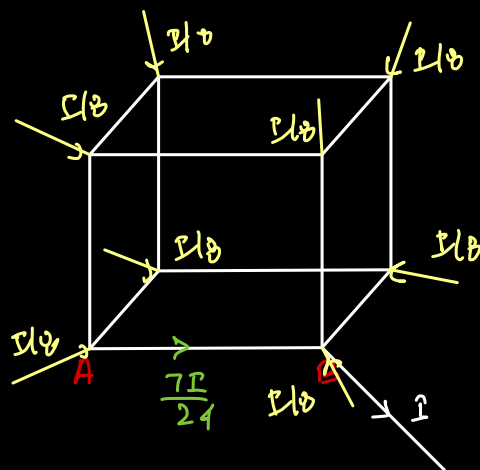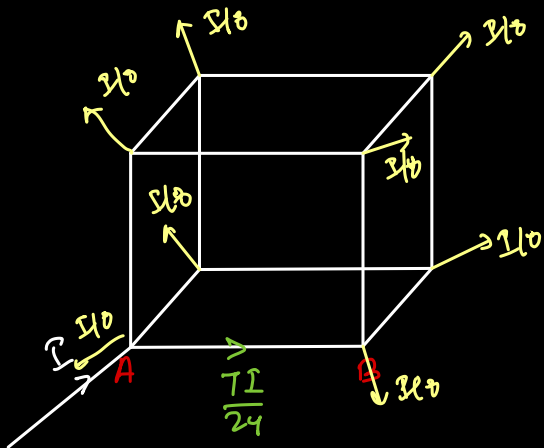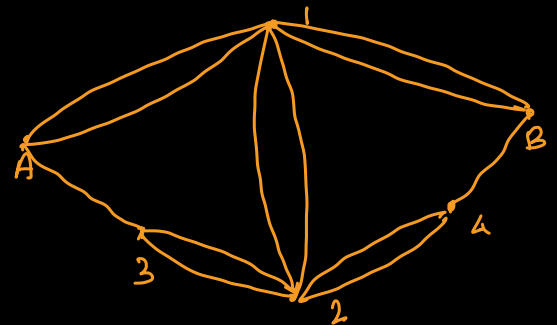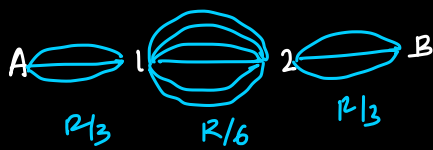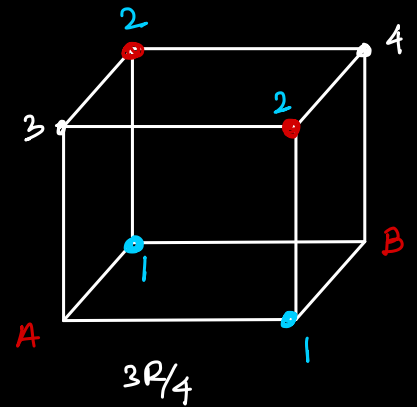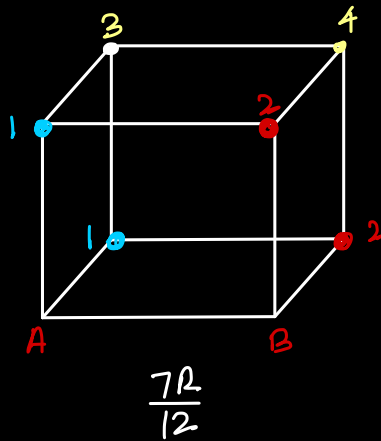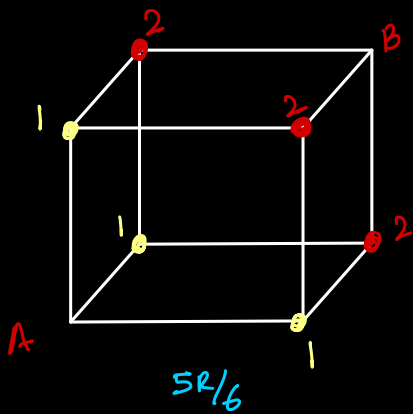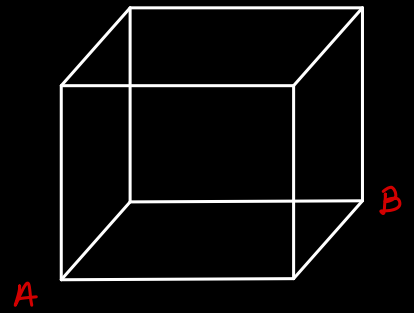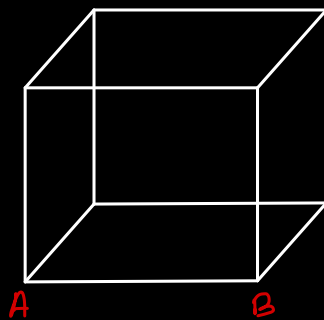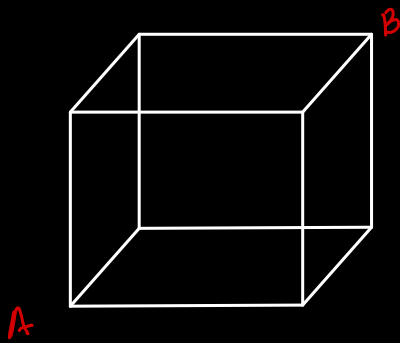

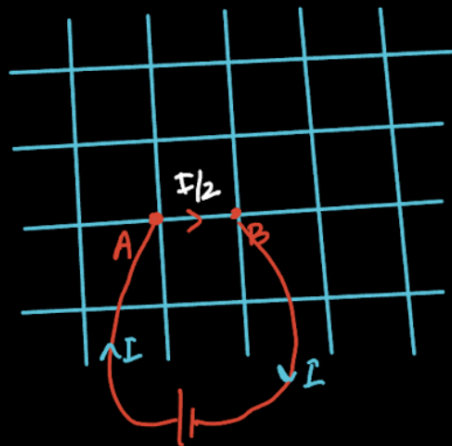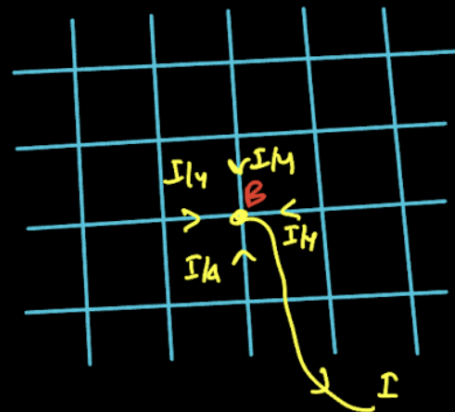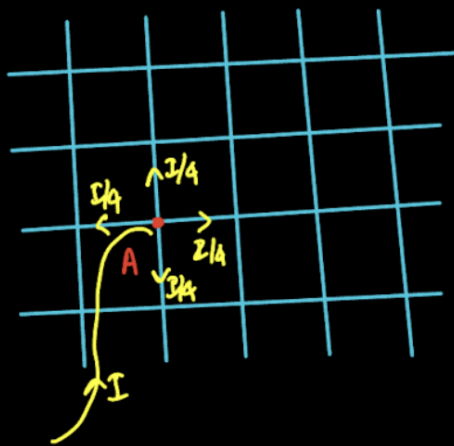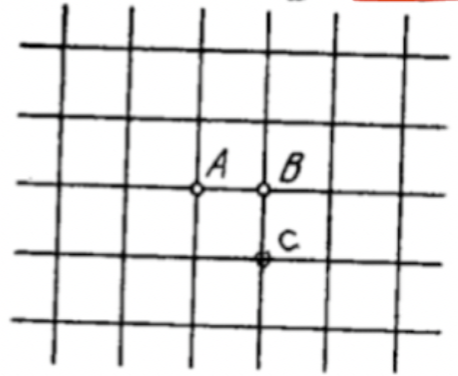3.153. There is an infinite wire grid with square cells (Fig. 3.38). The resistance of each wire between neighbouring joint connections is equal to R_0 . Find the resistance R of the whole grid between points A and B .

$$R_{AB} = \frac{R_0}{2}$$





Instruction. Make use of principles of symmetry and superposition.



$$\mathcal{E} = I R_{eq}$$

$$\mathcal{E} = I R/2$$


$$R_{eq} = R/2$$

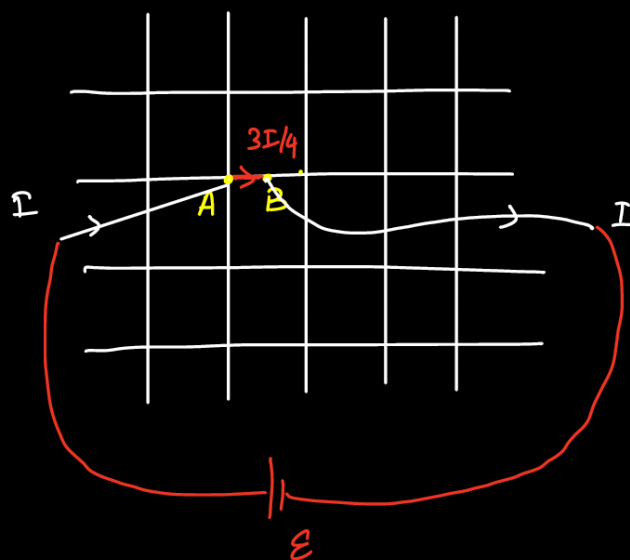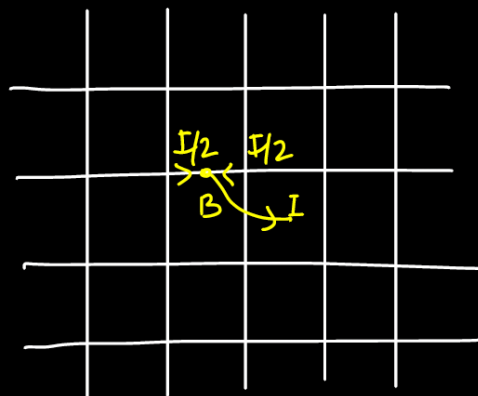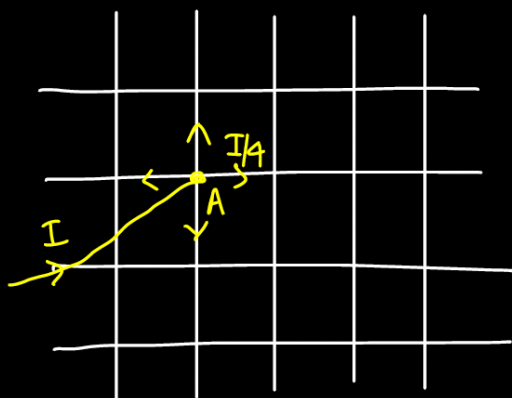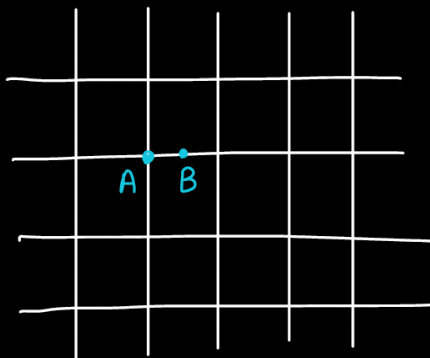

$$\mathcal{E} = \frac{3I}{4} \cdot \frac{R}{2} = IR_{eq}$$


$$R_{eq} = \frac{3R}{8}$$

Ex.

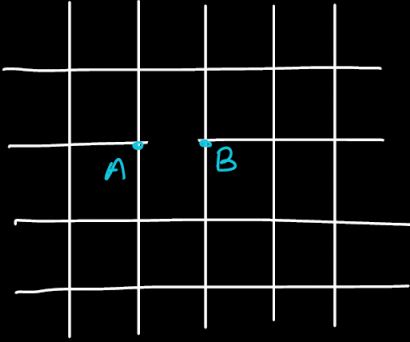

method 1


$$R_{AB} = R'$$

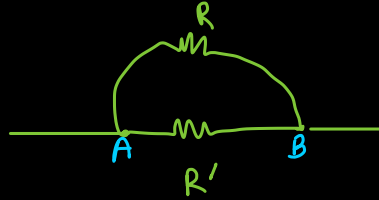


$$\frac{RR'}{R+R'} = \frac{R}{2}$$

$$R' = R$$

method 2

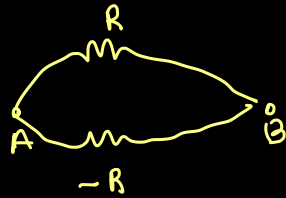


$$R_{eq} = \infty$$

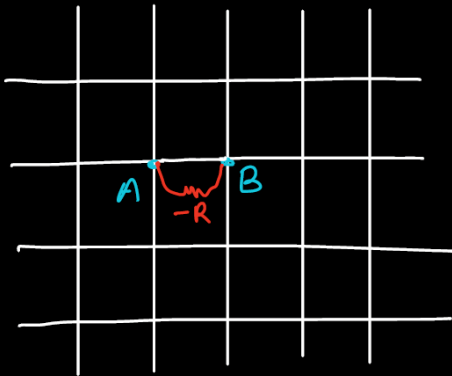

$$\Rightarrow R_{AB} = \frac{(R/2)(-R)}{(R/2) - R} = R$$

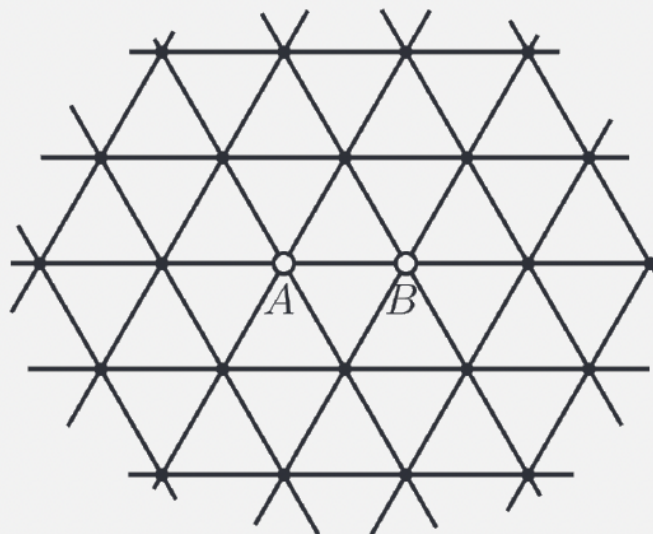pr 31. Determine the resistance between two neighbouring nodes in an infinite triangular lattice, as shown in the figure below. The resistance of the wire connecting any two neighbouring nodes is $1\ \Omega$.
Instructions: Let C be a node that is infinitely far from nodes A and B . Now consider the currents flowing between these nodes.




Ans: $R/3$

pr 33. Solve Problem 31 if the wire connecting nodes A and B is cut (i.e. current cannot flow through that wire).

Ans: $R/2$


Infinite ladder circuits

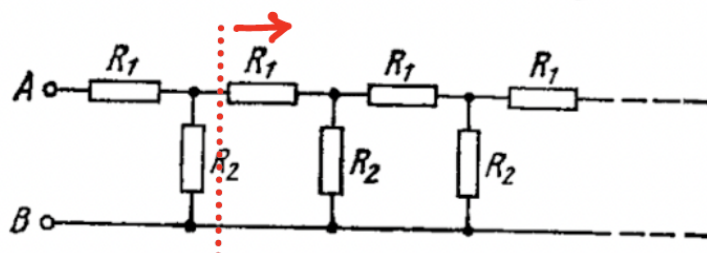3.152. Fig. 3.37 shows an infinite circuit formed by the repetition of the same link, consisting of resistance $R_1 = 4.0\ \Omega$ and $R_2 = 3.0\ \Omega$. Find the resistance of this circuit between points A and B .





Ans: $6\ \Omega$

$$R_{AB} = R$$

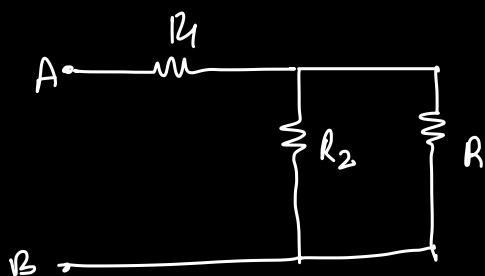


$$\left\{ \frac{R R_2}{R + R_2} \right\} + R_1 = R$$

Ex Find R_{eq} across AB

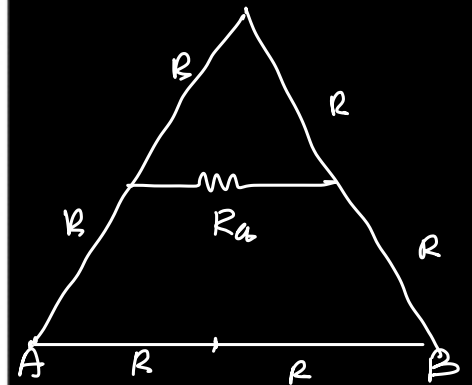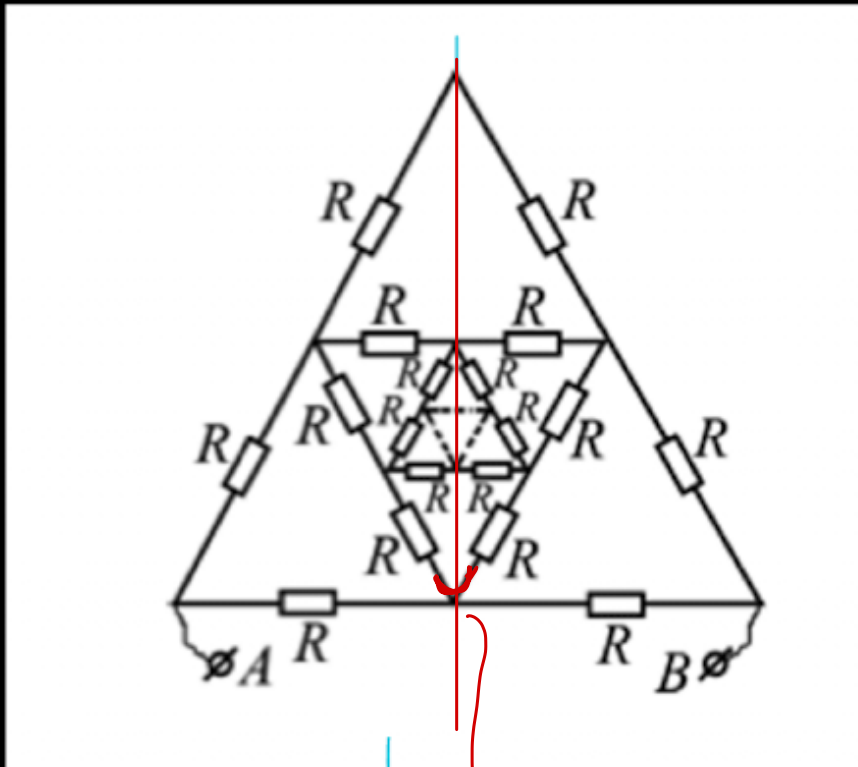


$$R_{eq} = \frac{2R}{\sqrt{3}}$$


node can be detached

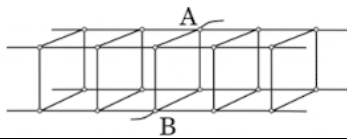

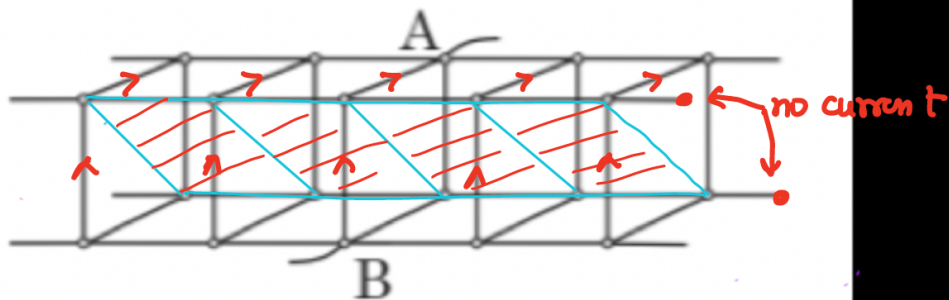
20. The network shown consists of an infinitely large number of identical sections. Resistance of each branch is R . Find resistance of the whole network measured between the terminals A and B.



Ans $\frac{R}{\sqrt{3}}$

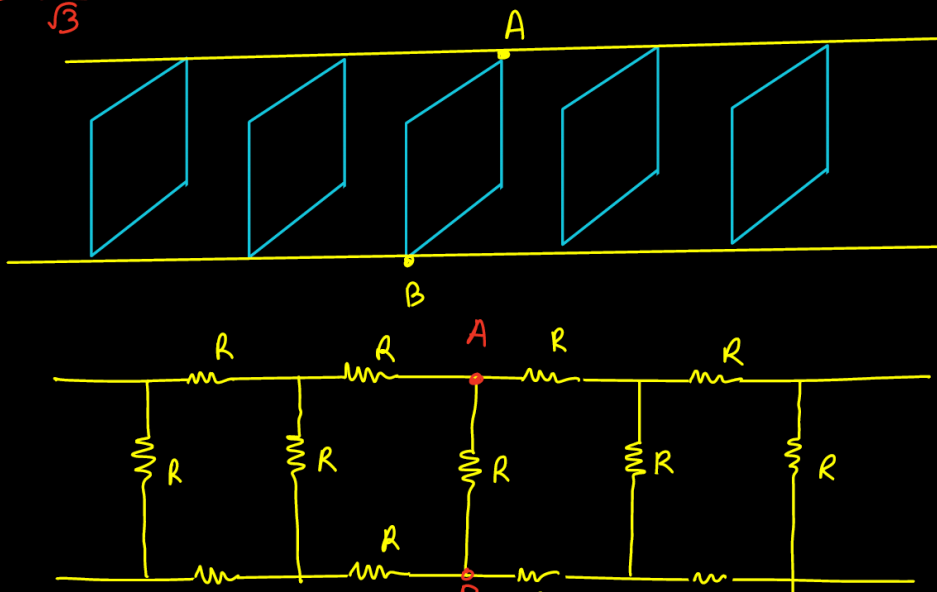


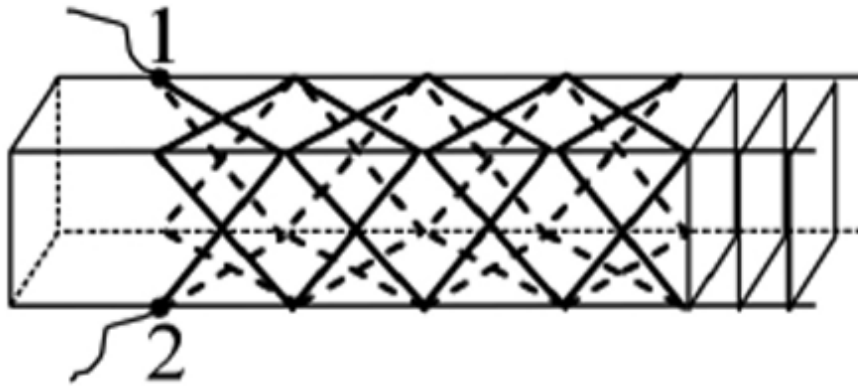Problem 66. (MOSH, 2010, 11) Eight identical long wires are wound around a long (semi-infinite) wooden block. The beginnings of these wires are connected in pairs, as shown in the figure. Find the resistance R_{12} between points 1 and 2 of this infinite "stocking-like" chain pulled over the block, if the resistance of a wire segment located between two adjacent intersections of wires is equal to R . There is electrical contact at all intersection points between the wires.



Ans: $R\sqrt{2}$

Batteries / cells

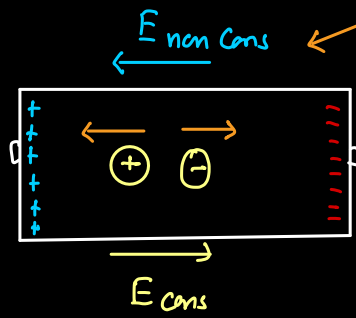

Electric field inside cell is non electrostatic





$$\text{Emf of battery } \mathcal{E} = \int \vec{E}_{\text{non cons}} \cdot d\vec{l}$$

$$\text{potential difference } \Delta V = - \int E_{\text{cons}} \cdot d\vec{l}$$

for an ideal battery

$$\Delta V = \mathcal{E}$$

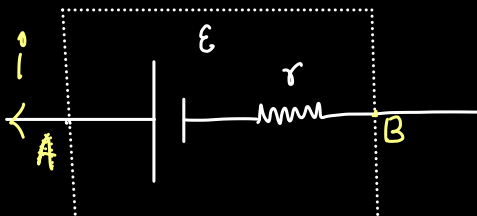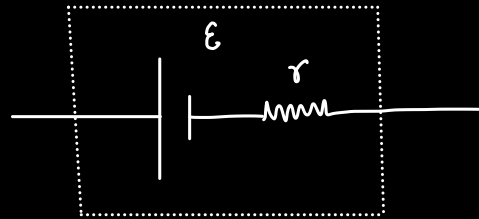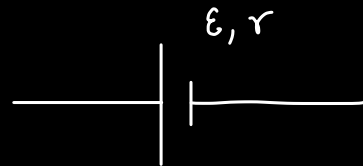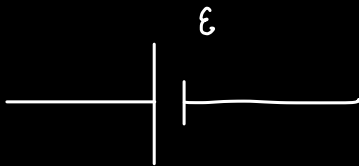
Non ideal battery, battery with internal resistance



$$V_A - \mathcal{E} + ir = V_B$$

$$V_A - V_B = \mathcal{E} - ir$$

Battery supplies energy

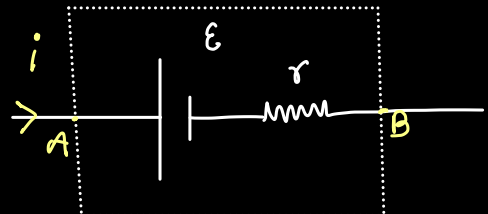


$$V_A - \mathcal{E} - ir = V_B$$

$$V_A - V_B = \mathcal{E} + ir$$

Battery absorbs energy

Combination of batteries


Batteries in series

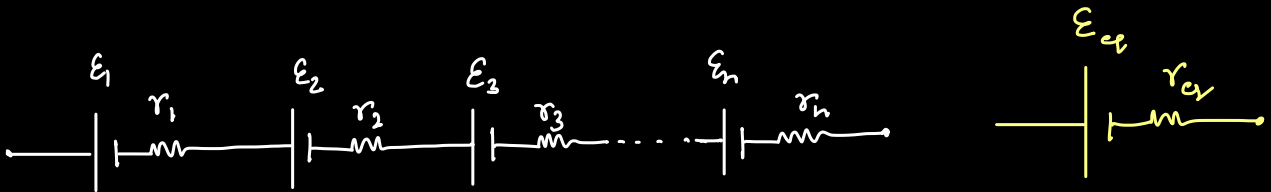

$$\mathcal{E}_q = \sum \mathcal{E}_i$$


$$r_q = \sum r_i$$

Batteries in parallel

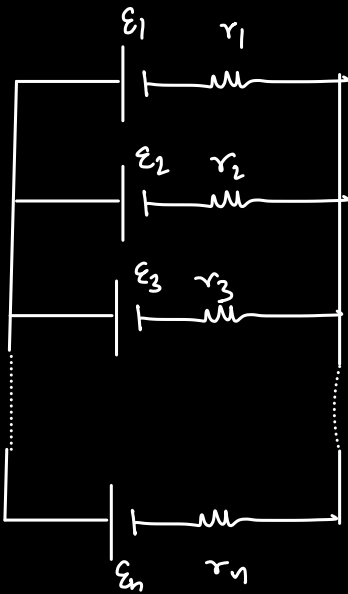


$$\mathcal{E}_q = \frac{\frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} + \dots + \frac{\mathcal{E}_n}{r_n}}{\frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}}$$
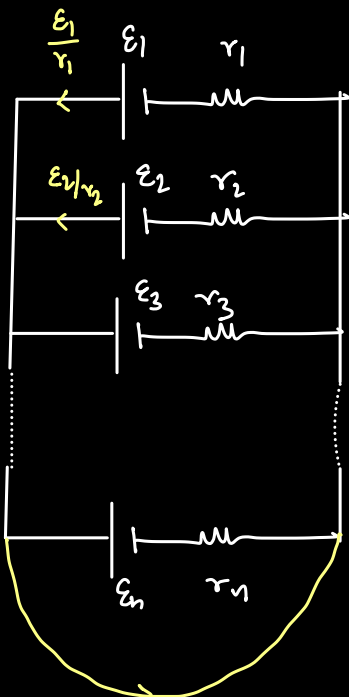
$$\frac{1}{r_q} = \frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}$$



$$i = \frac{\mathcal{E}_q}{r_q} = \frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} + \dots + \frac{\mathcal{E}_n}{r_n}$$

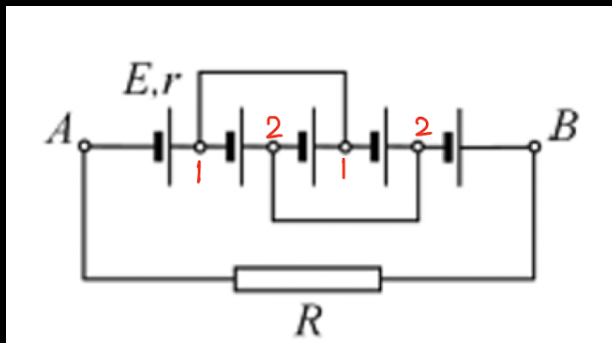PROBLEM 12. (Moscow School of Electrical Engineering, 2017, 11) Find the current I through a resistor with a resistance $R = 5 \text{ Ohm}$ in the circuit shown in the figure. All sources are the same and have an EMF $E = 15 \text{ V}$ and an internal resistance $r = 2 \text{ Ohm}$. Neglect the resistance of the connecting wires.



Ans: $\frac{7E}{3R+7r}$

