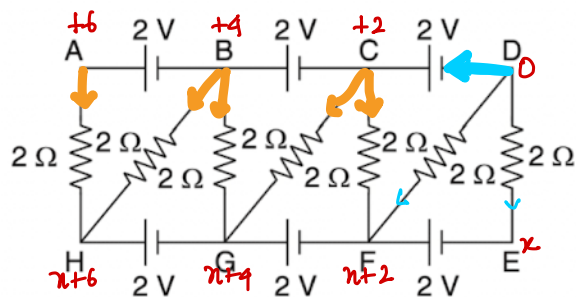


In given circuit, 7 resistors $2\ \Omega$ each and 6 batteries of 2 V each, are joined together.




The current through branch BG is:

- (a) 1 A (b) 0.2 A
(c) 0.4 A (d) 0.6 A

At D $\frac{0-n}{2} + \frac{0-(n+2)}{2} + \frac{-n}{2} - \frac{(n+2)}{2} - \frac{n}{2} - \frac{(n+2)}{2} - \frac{n}{2} = 0$

$$x = -\frac{6}{7}$$

Problems related to Symmetry in circuits


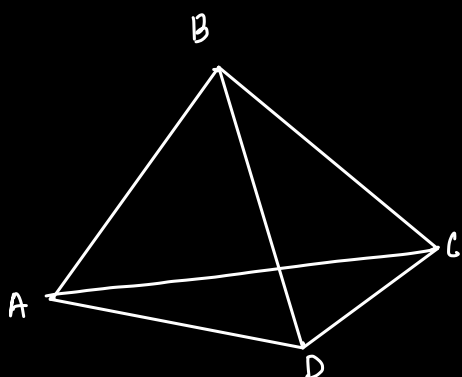


Each side has a resistance R

Find the equivalent resistance across A & B

method 1


flatten it

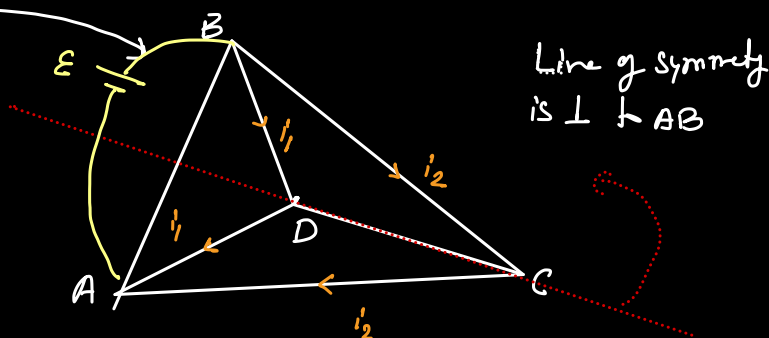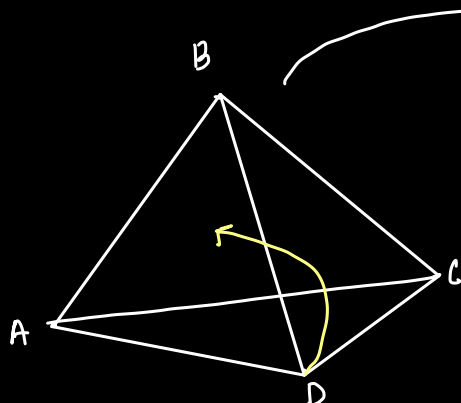

Line of symmetry is $\perp$ to AB

By symmetry $i_{BD} = i_{DA} \Rightarrow i_{CD} = 0$
 $i_{BC} = i_{CA}$


we can remove CD

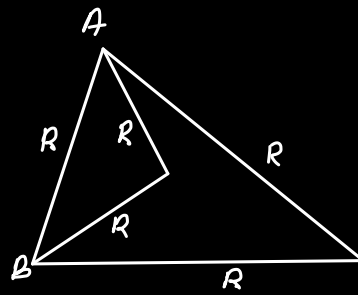

$$R_{eq} = \frac{R}{2}$$

method 2

Method of equipotential points

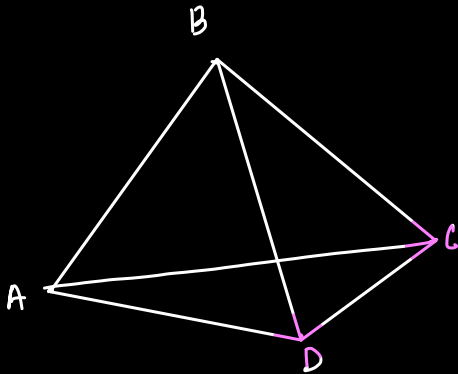

paths of C & D to A are identical


+

paths of C & D to B are identical


↓

C & D are at same potential

Ex

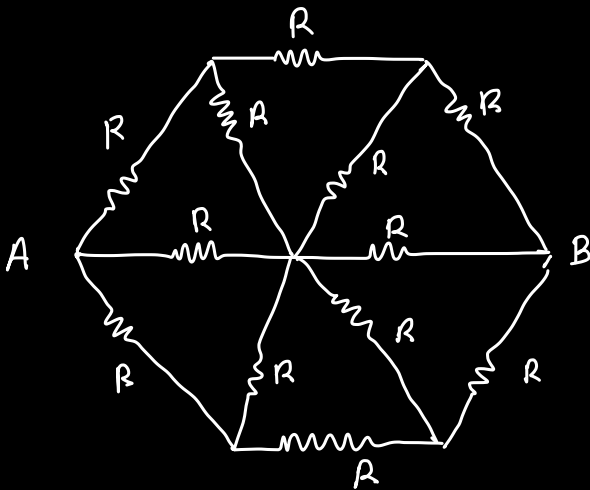


Find eq. resistance about AB

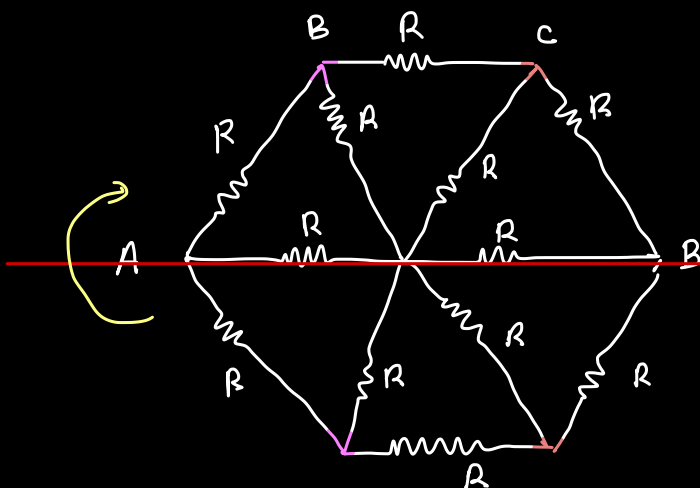

line of symmetry passes through AB


FOLDING SYMMETRY

After folding

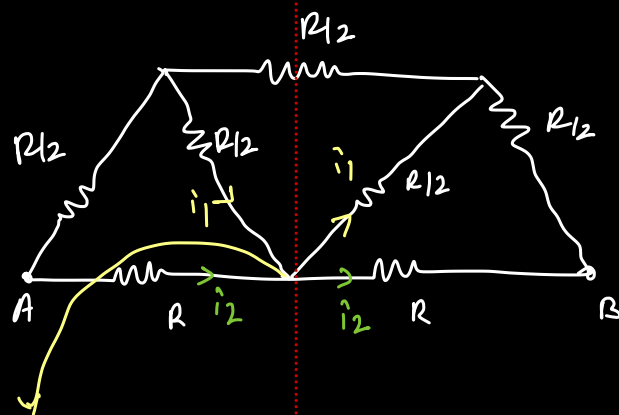


Junction can
be
removed

→ line of symmetry $\perp$ to AB

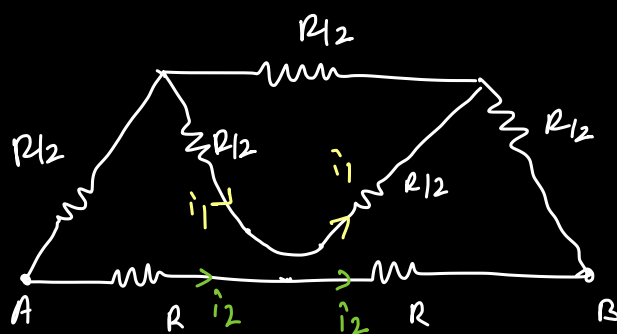

$$R_{eq} = \frac{4R}{5}$$

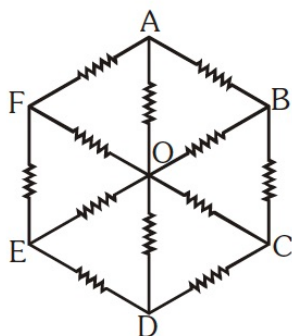Twelve wires of equal resistance R are placed in a given arrangement as shown in figure. Then find



2. Equivalent resistance between A & B is


- ✓ (A) $\frac{11R}{20}$ (B) $\frac{10R}{20}$ (C) $\frac{R}{20}$ (D) $\frac{3R}{2}$

3. Equivalent resistance between A & C is

- ✓ (A) $\frac{3R}{4}$ (B) $\frac{R}{4}$ (C) $\frac{5R}{6}$ (D) $\frac{3R}{5}$


4. Equivalent resistance between A & O is

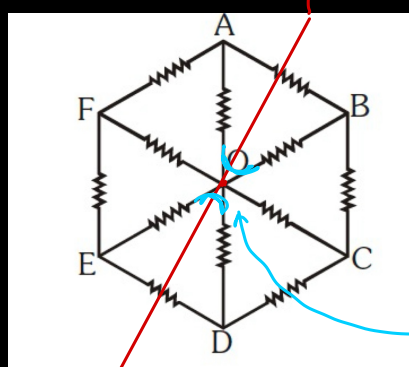- (A) $\frac{19R}{41}$ (B) $\frac{20R}{41}$ (C) $\frac{18R}{23}$ ✓ (D) $\frac{9R}{20}$






line of symmetry $\perp$ to AB

these junctions can be disconnected

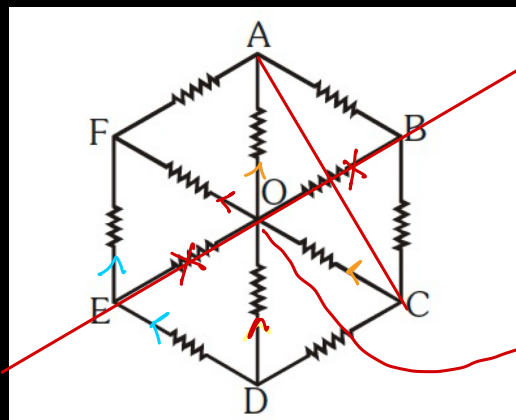



junction can be disconnected




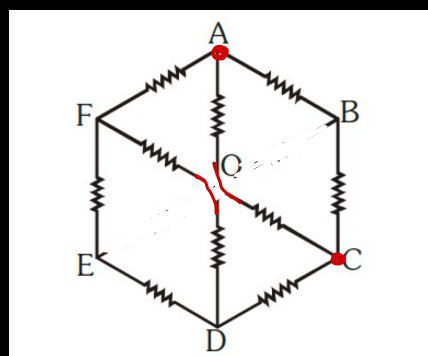


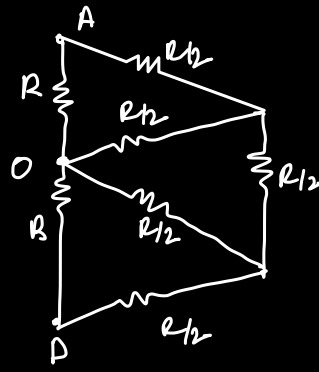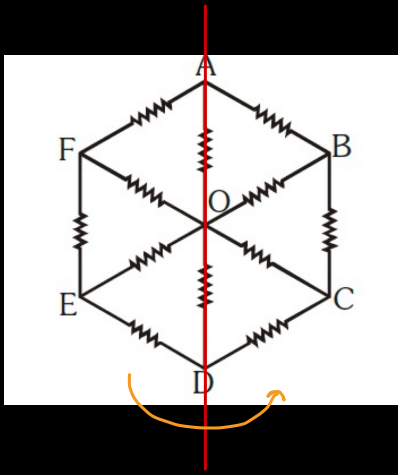


line of symmetry pass through
A to fold in symmetry

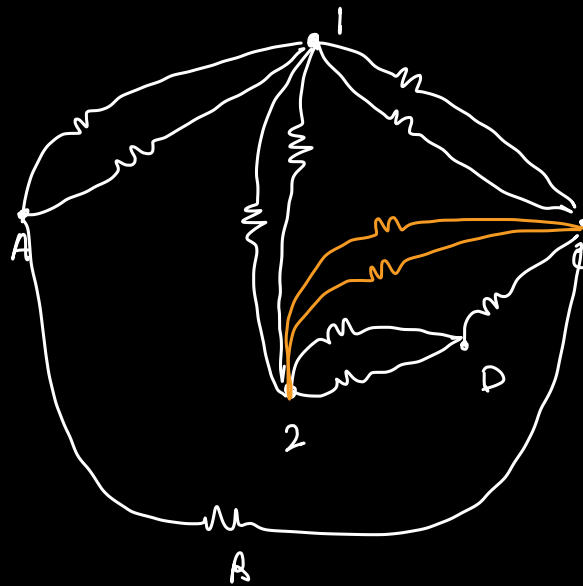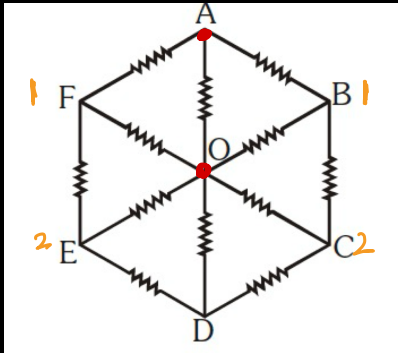method of equipotentials / redraws the circuit




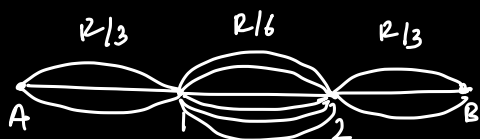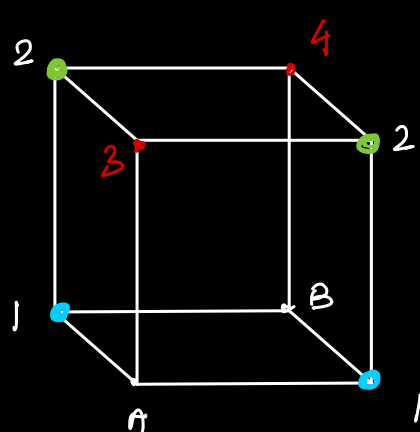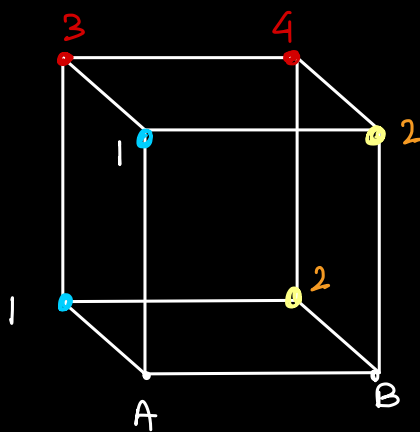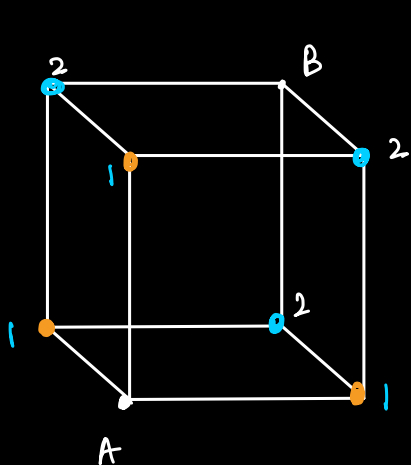

$$R_{eq} = \frac{5R}{6}$$

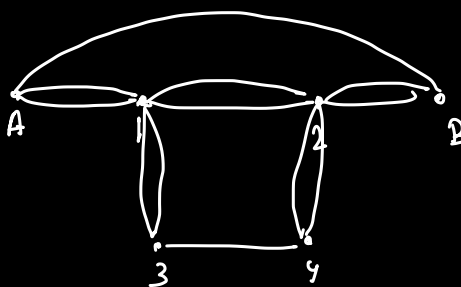


$$R_{eq} = \frac{7R}{12}$$

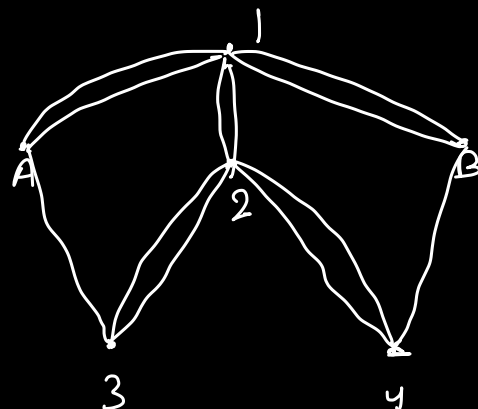

$$R_{eq} = \frac{3R}{4}$$


Infinite ladder circuits

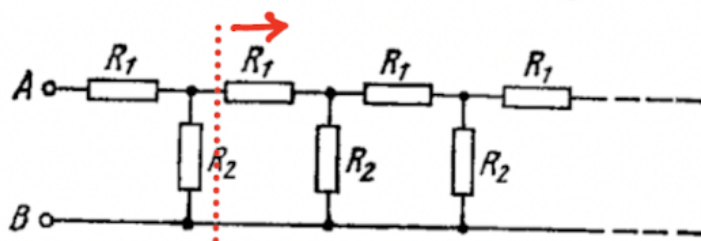3.152. Fig. 3.37 shows an infinite circuit formed by the repetition of the same link, consisting of resistance $R_1 = 4.0 \Omega$ and $R_2 = 3.0 \Omega$. Find the resistance of this circuit between points A and B.





Ans: 6Ω

If equivalent resistance is R

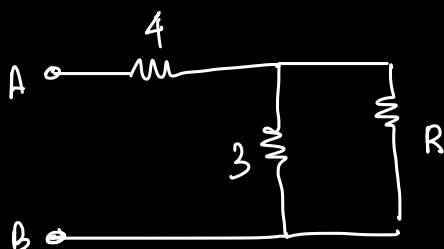

$$\frac{3R}{3+R} + 4 = R$$

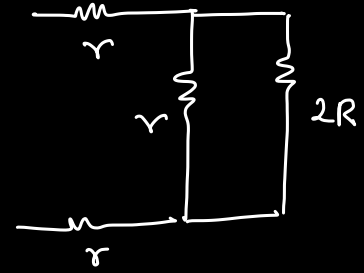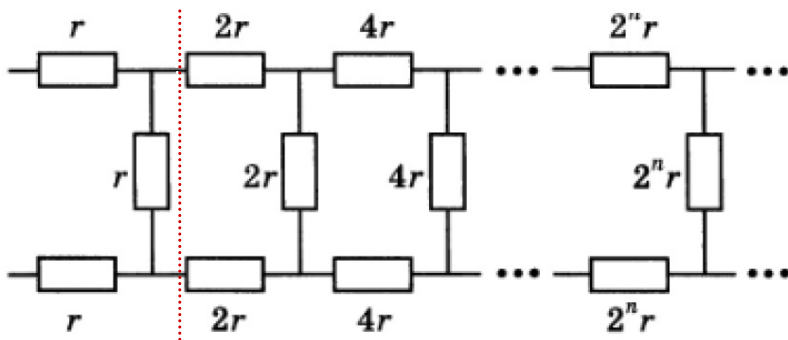

$$\frac{2Rr}{2R+r} + 2r = R$$

HW

19. Find equivalent resistance between the terminals A and B of the following infinite ladder networks.

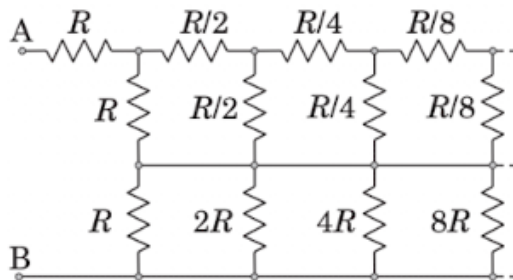


Figure-I



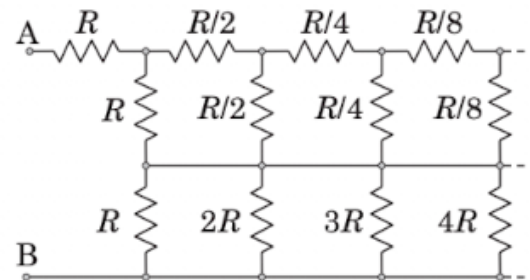
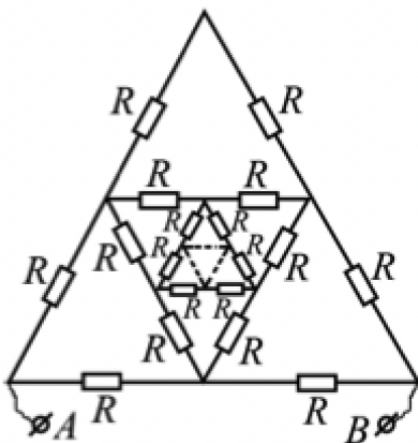


Figure-II

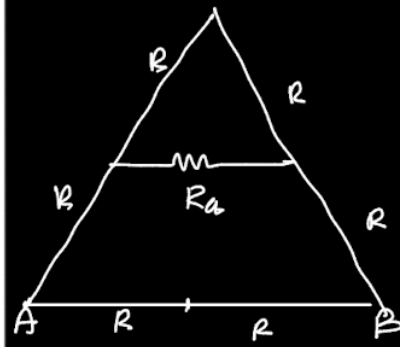"PROBLEM 71. (MOSH, 2010, 10) Find the resistance between terminals A and B of the infinite circuit shown in the figure. The resistance of each resistor is equal to R."






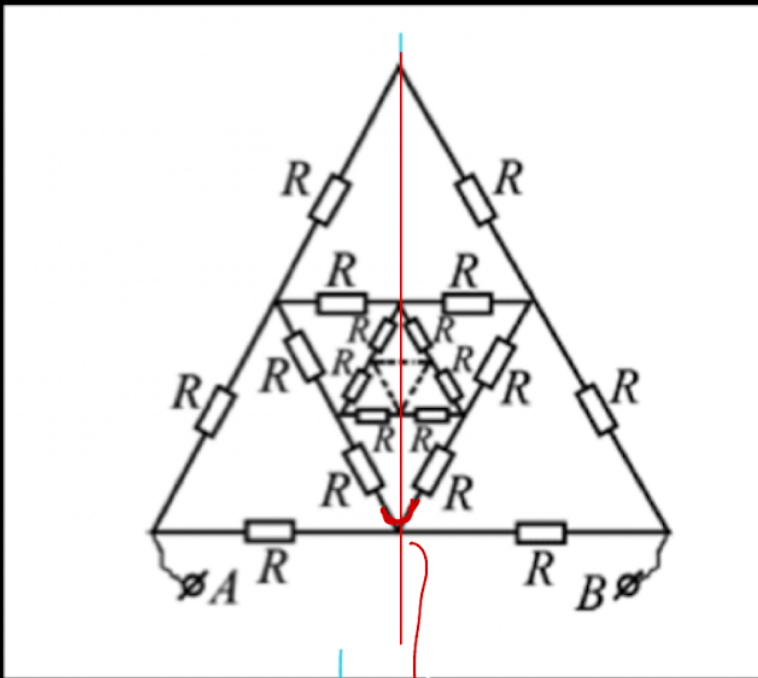


$$R_g = \frac{2R}{\sqrt{3}}$$

Infinite grid circuits

Find R_{eq}

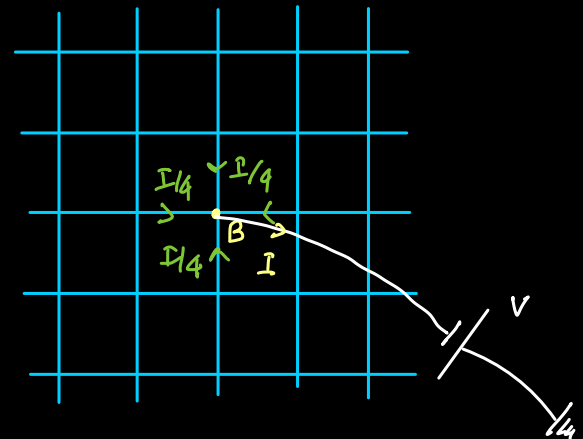
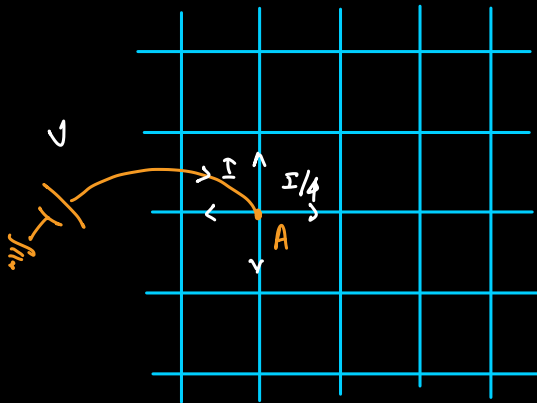
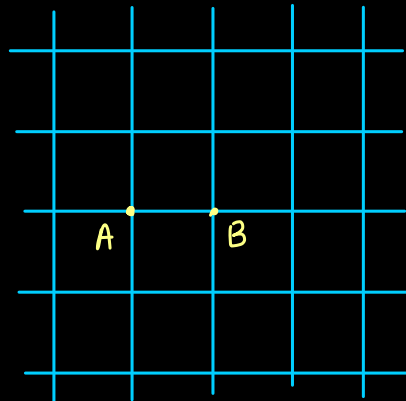


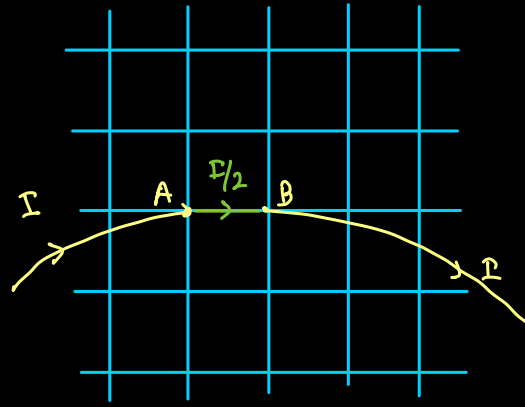

$$\Delta V_{A \rightarrow B} = I R_q = I/2 R$$


$$R_q = \frac{R}{2}$$

Elementary example of superposition

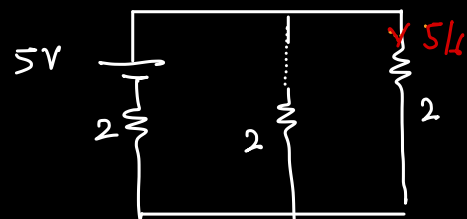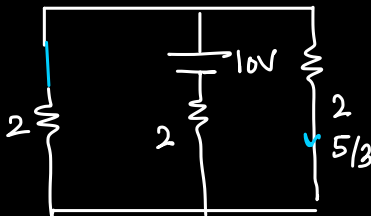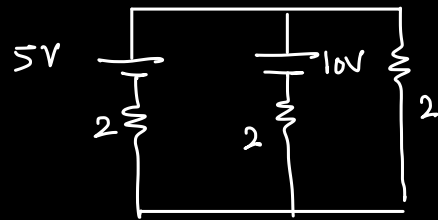


find current by each source individually and then
superimpose the current to get the current as $\frac{5}{2} A$

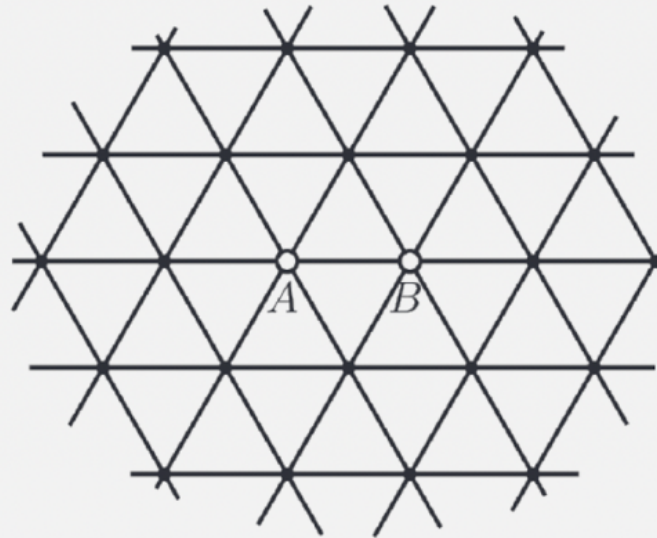pr 31. Determine the resistance between two neighbouring nodes in an infinite triangular lattice, as shown in the figure below. The resistance of the wire connecting any two neighbouring nodes is $1\ \Omega$. *Instructions:* Let C be a node that is infinitely far from nodes A and B . Now consider the currents flowing between these nodes.



Ans: $R/3$

Batteries/cells

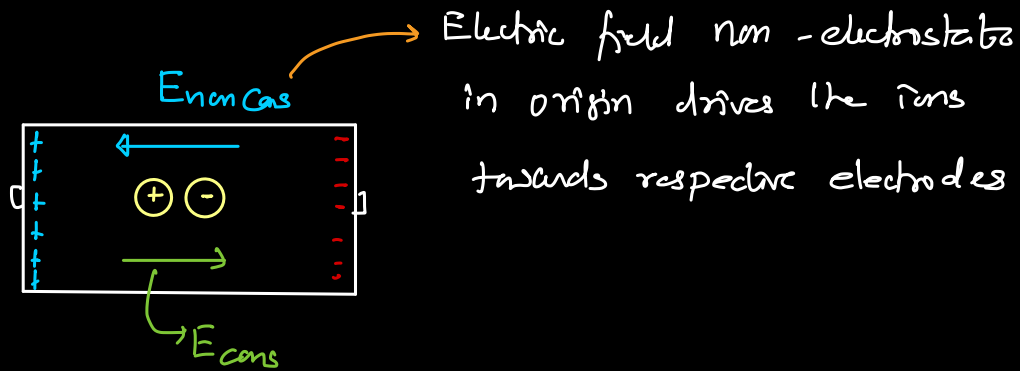

Emf of battery : Work done per unit charge by non conservative electric field in moving the charge from one electrode to other

$$\mathcal{E} = \int \vec{E}_{\text{noncons}} \cdot d\vec{l}$$




Potential difference across a battery


$$\Delta V = - \int \vec{E}_{\text{cons}} \cdot d\vec{l}$$

For ideal battery

$$\mathcal{E} = \Delta V$$

Non ideal battery

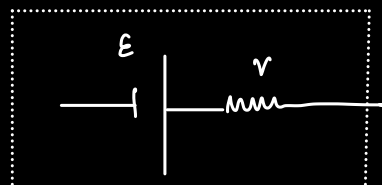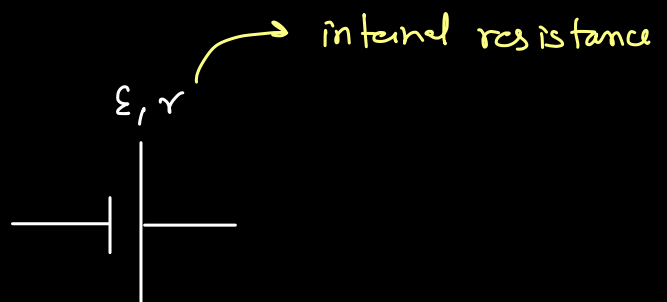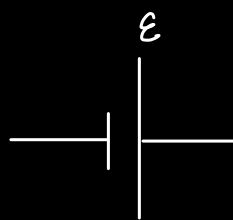


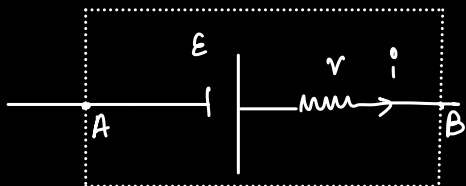

$$V_A + \varepsilon - ir = V_B$$

$$V_B - V_A = \varepsilon - ir$$

Battery is supplying energy to circuit

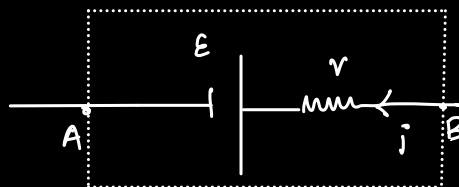


$$V_A + \varepsilon + ir = V_B$$

$$V_B - V_A = \varepsilon + ir$$

Battery is absorbing energy from circuit

Combination of batteries


Series

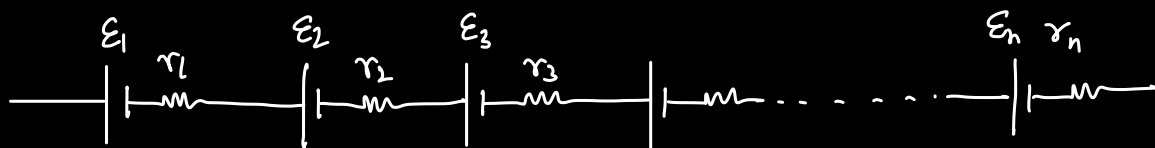

$$\varepsilon_q = \sum \varepsilon_i$$


$$r_q = \sum r_i$$

Parallel

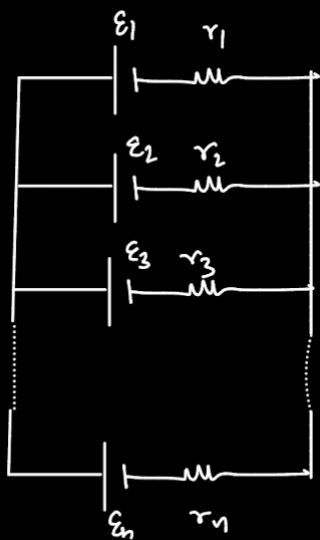


$$\varepsilon_q = \frac{\frac{\varepsilon_1}{r_1} + \frac{\varepsilon_2}{r_2} + \dots + \frac{\varepsilon_n}{r_n}}{\frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}}$$
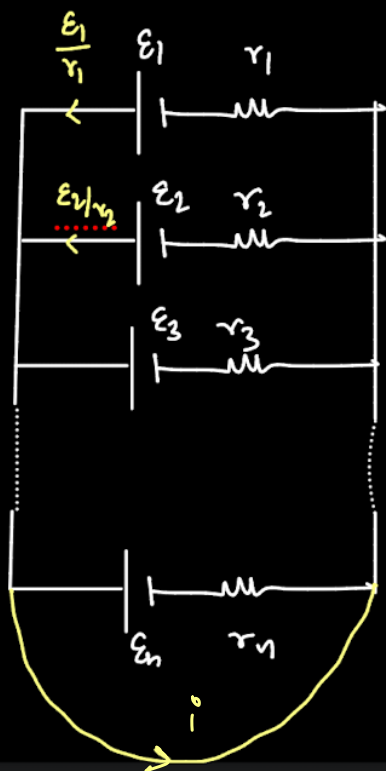
$$\frac{1}{r_q} = \frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}$$



$$i = \frac{\mathcal{E}_q}{r_q} = \frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} + \dots + \frac{\mathcal{E}_n}{r_n}$$

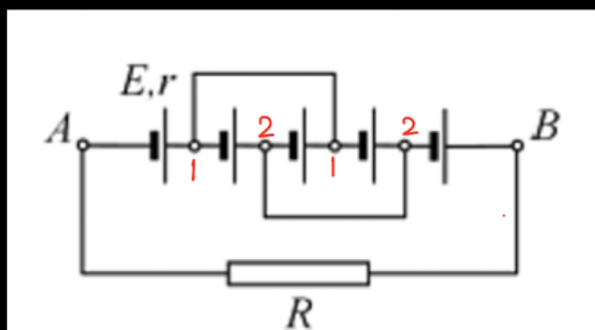PROBLEM 12. (Moscow School of Electrical Engineering, 2017, 11) Find the current I through a resistor with a resistance $R = 5 \text{ Ohm}$ in the circuit shown in the figure. All sources are the same and have an EMF $E = 15 \text{ V}$ and an internal resistance $r = 2 \text{ Ohm}$. Neglect the resistance of the connecting wires.



Ans: $\frac{7E}{3R+7r}$

