
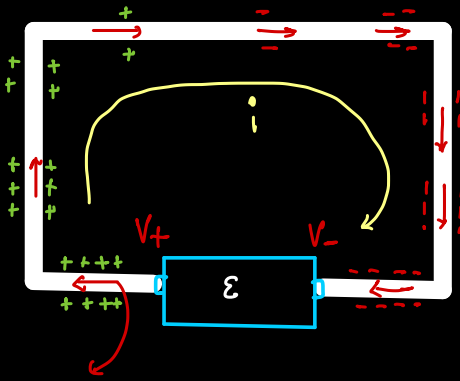


Electric Circuits

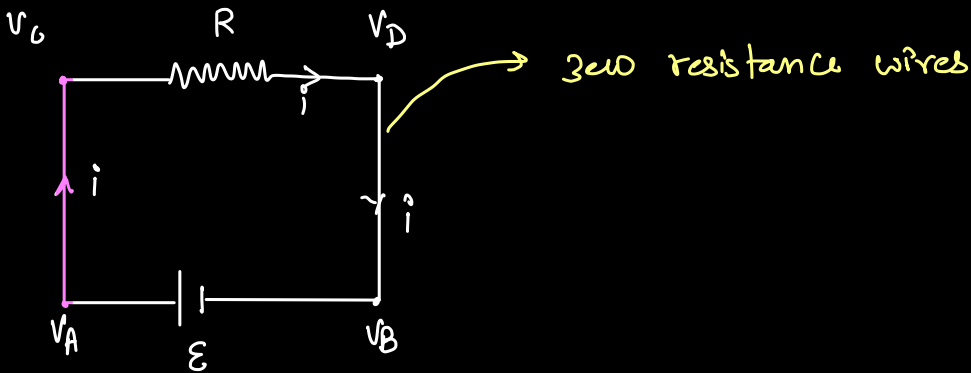

Emf of battery $\mathcal{E} = V_+ - V_-$

Electric field is created due to charges appearing on the surface of the wire



Ohm's law

$$V_A - V_C = iR \rightarrow 0$$

$$V_A = V_C$$

potential at every point on a zero resistance wire is same.



For R

$$V_C - V_D = iR$$

$$V_A - V_B = iR$$

$$\boxed{\mathcal{E} = iR}$$

Resistances in Series

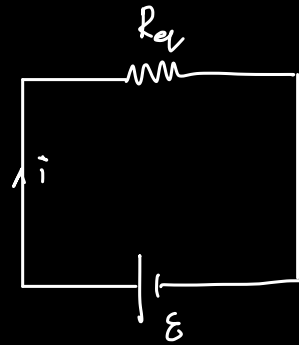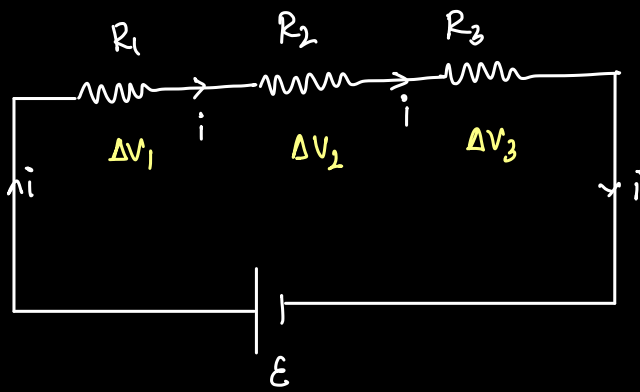


$$\Delta V_1 + \Delta V_2 + \Delta V_3 = \varepsilon$$




$$iR_1 + iR_2 + iR_3 = iR_{eq}$$

$$R_{eq} = \sum R_i$$

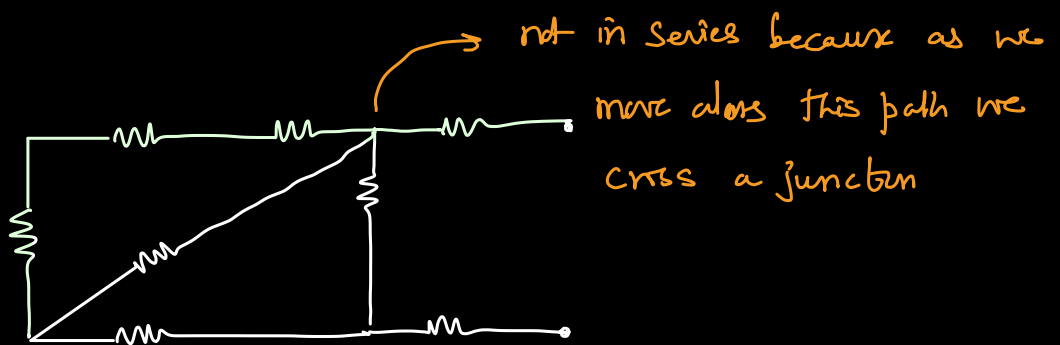When can we say that resistances are in series?



Resistances in parallel

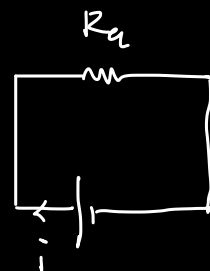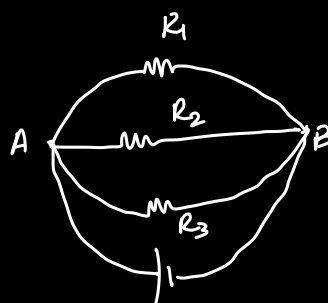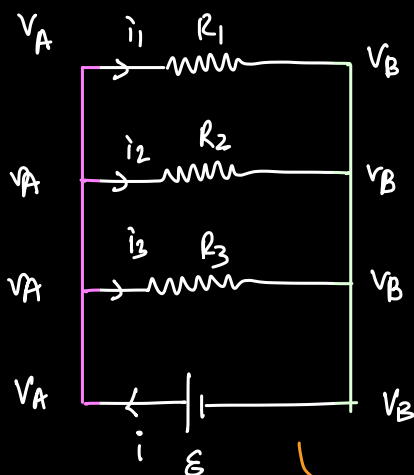

Same

Potential difference across all resistors is equal


$$i = i_1 + i_2 + i_3$$

$$\frac{E}{R_q} = \frac{E}{R_1} + \frac{E}{R_2} + \frac{E}{R_3}$$

$$\boxed{\frac{1}{R_q} = \sum \frac{1}{R_i}}$$

Note:

(i)

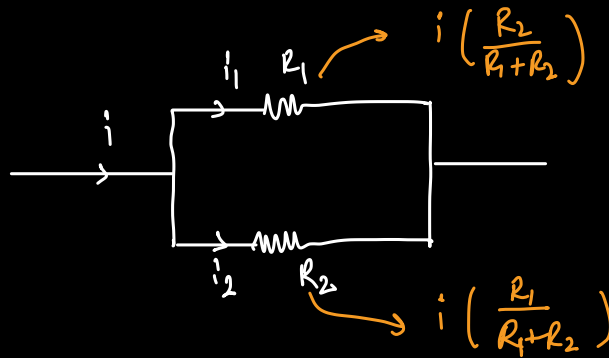


$$\Delta V_1 = \Delta V_2$$

$$i_1 R_1 = i_2 R_2$$


$$\frac{i_1}{i_2} = \frac{R_2}{R_1}$$

Current i is divided in reverse ratio of resistances

(ii) Short circuit

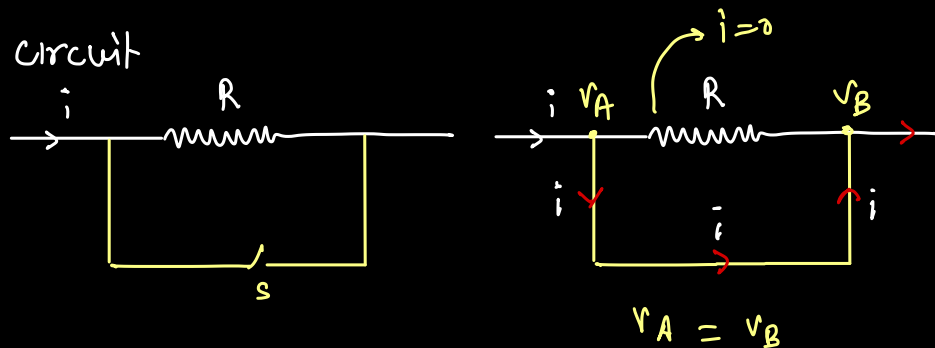

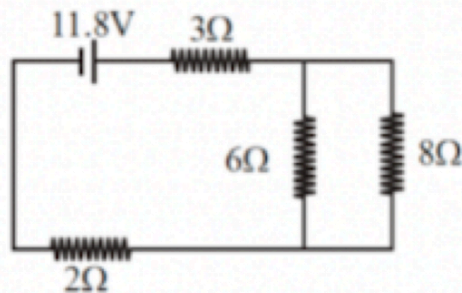In the network, the current in the resistor 6Ω is :




(A) $\frac{7}{5}$ A


(B) $\frac{4}{5}$ A

(C) $\frac{3}{5}$ A

(D) zero

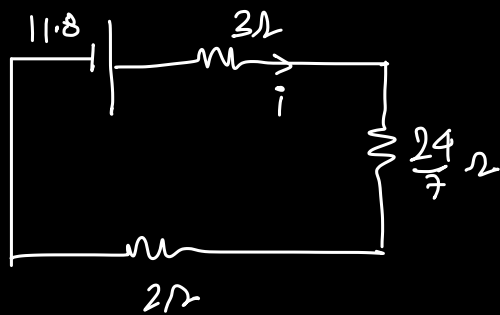

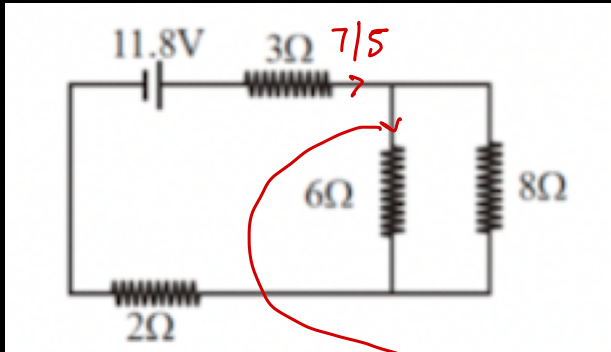
$$i = \frac{11.8}{\frac{24}{7} + 2} = \frac{7}{5} A$$



$$\frac{7}{5} \left(\frac{8}{8+6} \right) = \frac{4}{5} A \text{ Ans}$$

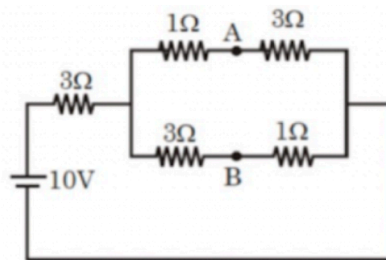A battery of emf 10V is connected to resistances as shown in figure. The potential difference $V_A - V_B$ between the points A and B is :-




(A) 2V

(B) -2V

(C) 5V

(D) $\frac{20}{11} V$


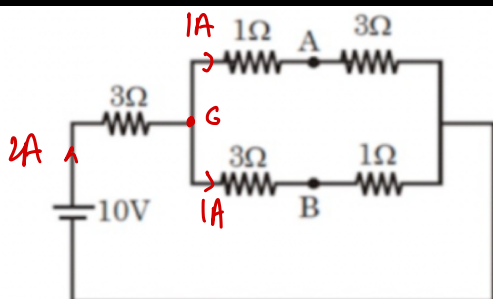


$$V_C - V_B = 1(3)$$

$$- V_C - V_A = 1(1)$$

$$V_A - V_B = 3 - 1 = 2$$

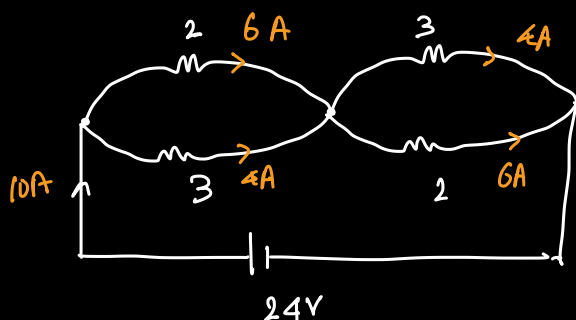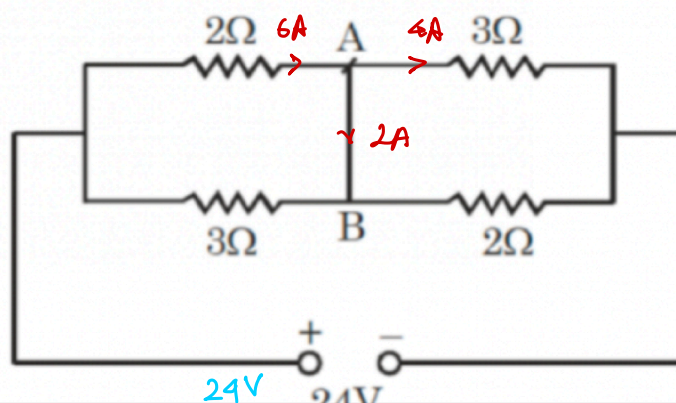
Consider circuit as shown in figure. The current through wire AB is



$$i = \frac{24}{R_{eq}} = 10A$$

$\frac{12}{5} \rightarrow R_{eq}$

For the circuit shown in figure

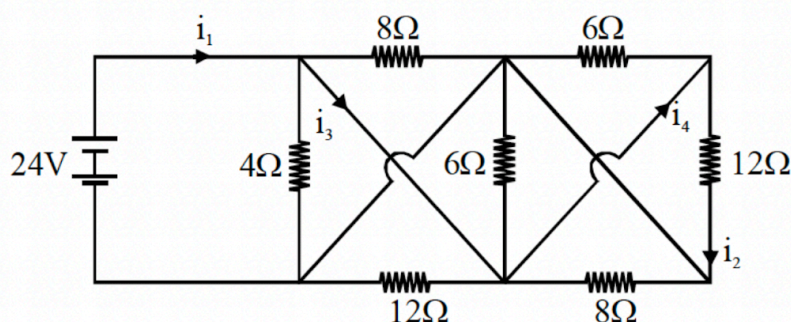


~~(A)~~ $i_1 = 24A$

~~(B)~~ $i_2 = 2A$

~~(C)~~ $i_3 = 15A$

~~(D)~~ $i_4 = 6A$



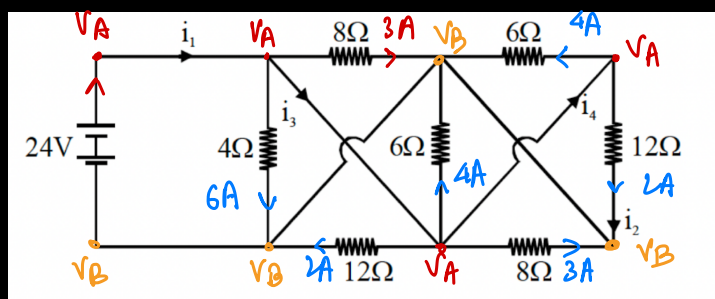


$$\frac{1}{R_{eq}} = \frac{2}{8} + \frac{2}{6} + \frac{2}{12} + \frac{1}{4}$$

$$R_{eq} = 1\Omega$$


$$i_1 = \frac{\mathcal{E}}{R_{eq}} = \frac{24}{1} = 24A$$

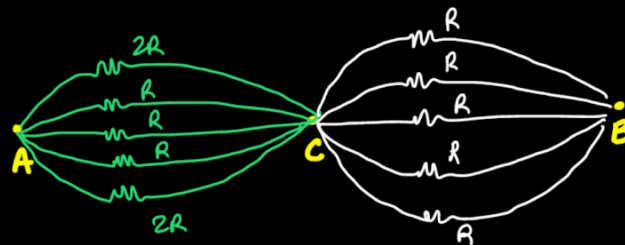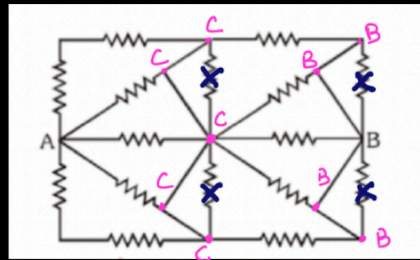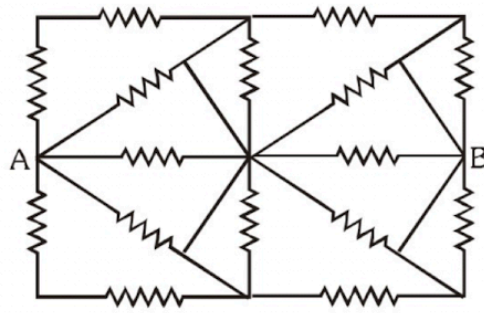In the given circuit all resistors are identical. Each resistance is equal to 20Ω . Find the equivalent resistance between A & B in Ω .



Kirchoff's laws

(i) Kirchoff's voltage law (KVL)




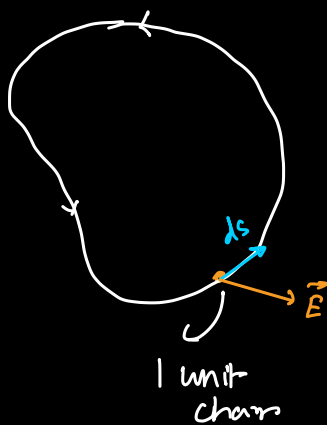


$$\oint (1) \vec{E} \cdot d\vec{s} = \int -dV = 0$$

↓
Total work done by electric field on a closed path is zero

Total change in potential in a closed path is zero

Sign Conventions

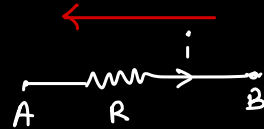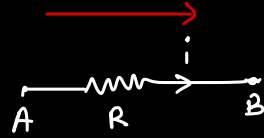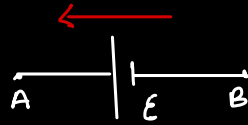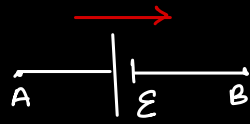

Change in potential

$$-E$$

pot dec since goes
from high pot to lower
pot

$$+E$$

pot inc since goes
from lower pot to higher
pot


$$-iR$$

In direction of current
pot decreases

$$+iR$$

opp to direction of current
pot increases

Kirchhoff's current law

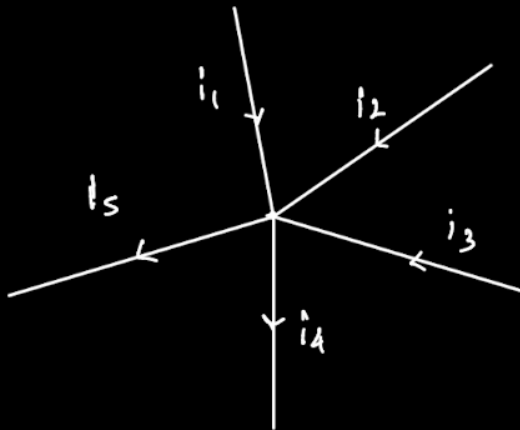



$$i_1 + i_2 + i_3 = i_4 + i_5$$

$$\sum i_{in} = \sum i_{out}$$

3.182. In the circuit shown in Fig. 3.45 the sources have emf's $\mathcal{E}_1 = 1.5 \text{ V}$, $\mathcal{E}_2 = 2.0 \text{ V}$, $\mathcal{E}_3 = 2.5 \text{ V}$, and the resistances are equal to $R_1 = 10 \Omega$, $R_2 = 20 \Omega$, $R_3 = 30 \Omega$. The internal resistances of the sources are negligible. Find:

(a) the current flowing through the resistance R_1 ;

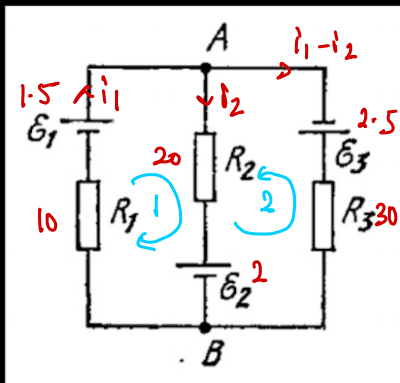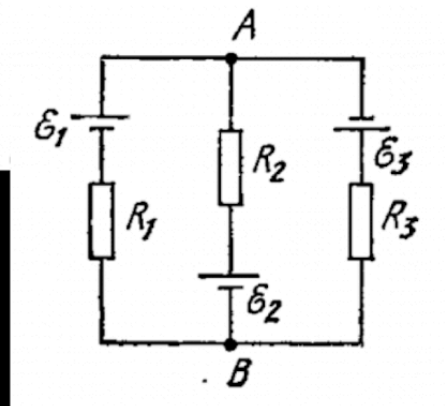(b) a potential difference $\varphi_A - \varphi_B$ between the points A and B.




$$V_A - i_2(20) - 2 = V_B$$

$$1) -10i_1 + 1.5 - 20i_2 - 2 = 0$$

$$2) + (i_1 - i_2)30 - 2.5 - i_2(20) - 2 = 0$$

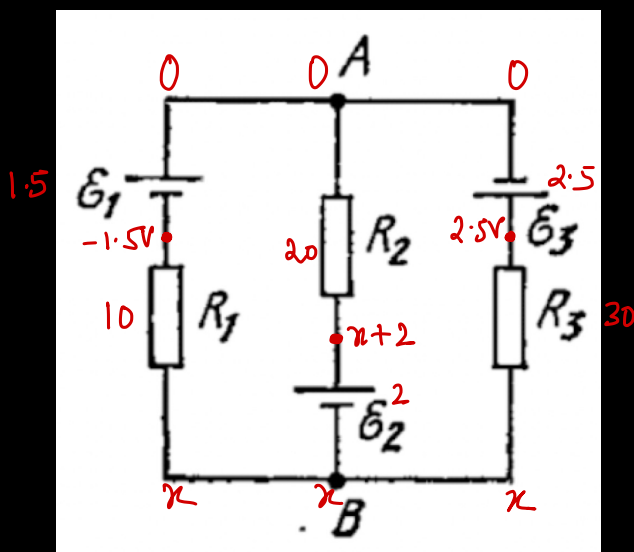Nodal Analysis / junction potential method




Step 1 Assign potential to all nodes or junctions

Step 2: Write KCL at B

Net outgoing current at B = 0

$$\frac{x - (-1.5)}{10} + \frac{(x+2) - 0}{20} + \frac{x - 2.5}{30} = 0$$

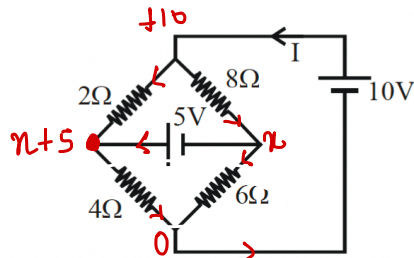The current supplied to the circuit by 10 V cell is I ampere. Assume both cells as ideal find 4I.



$$I = \frac{\frac{12}{5} + \frac{12+5}{5}}{\frac{6}{5} + \frac{4}{5}} = \frac{45}{20} = \frac{9}{4}$$

$$\frac{10 - (n+5)}{2} + \left(\frac{10-n}{8} - \frac{n-0}{6} \right) = \frac{(n+5)-0}{4}$$

current through 5V battery


$$5 - \frac{n}{2} - \frac{5}{2} + \frac{5}{4} - \frac{n}{8} - \frac{n}{6} = \frac{n}{4} + \frac{5}{4}$$

$$\frac{5}{2} = n \left(\frac{1}{4} + \frac{1}{2} + \frac{1}{8} + \frac{1}{6} \right)$$

$$\frac{5}{2} = n \left(\frac{6+12+3+4}{24} \right)$$

$$\frac{12}{5} = n$$

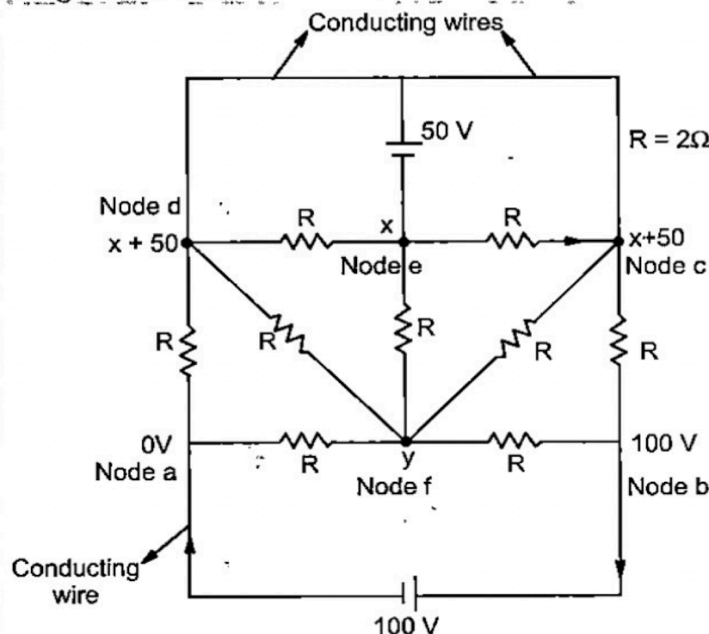In the given circuit we wish to determine the current through resistor given in box.



$$x = \frac{-25}{2}, \quad y = \frac{125}{2} \quad \text{and} \quad i = \frac{75}{2} \text{ A}$$

Solution:

Step-1: Assign voltage at all the nodes as shown in figure. Here x and y are unknown voltage at node e and f.

Step-2: Apply KCL at node f

$$\frac{y-100}{2} + \frac{y-(x+50)}{2} + \frac{y-x}{2} + \frac{y-(x+50)}{2} + \frac{y}{2} = 0 \quad \dots(1)$$


Step-3: Note that outgoing current at node a is equal to incoming current at node a, thus we get

$$\frac{100-(x+50)}{2} + \left(\frac{100-y}{2} \right) = - \left[\left(\frac{0-y}{2} \right) + \frac{0-(x+50)}{2} \right] \quad \dots(2)$$

Note that we require first two equations to get x and y.

Solve x and y to get current in R as $\frac{y-x}{2}$.
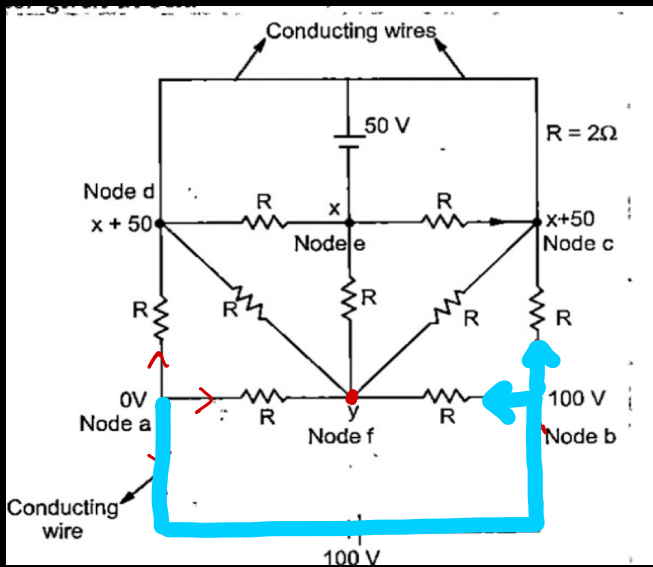
$$x = \frac{-25}{2}, \quad y = \frac{125}{2} \quad \text{and} \quad i = \frac{75}{2} \text{ A}$$



Node f

$$\frac{y-0}{R} + \frac{y-100}{R} + \frac{y-x}{R} + \frac{y-(x+50)}{R} \times 2 = 0$$


$$5y - 3x = 200$$

Node a

$$\frac{0-(x+50)}{R} + \frac{0-y}{R} + \frac{100-(x+50)}{R} + \frac{100-y}{R} = 0$$

$$x + y = 50$$

Wheatstone bridge

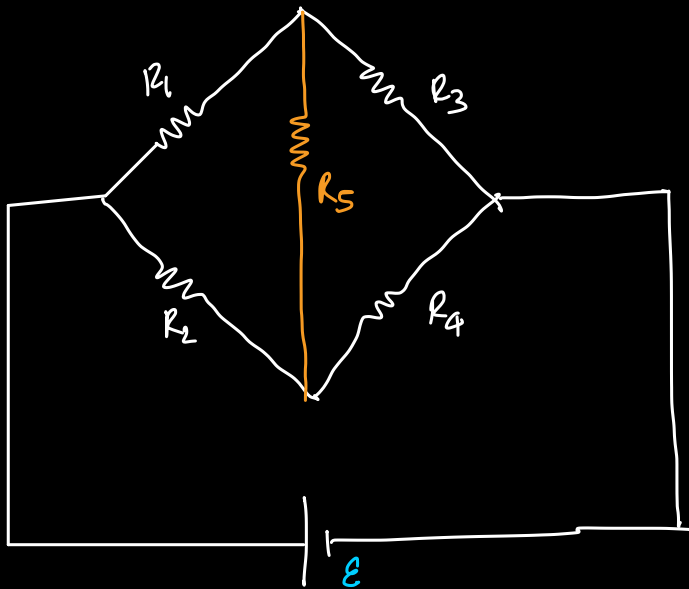


If



$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

Then the circuit is called a balanced Wheatstone bridge
current in R_5 is zero


Ex.

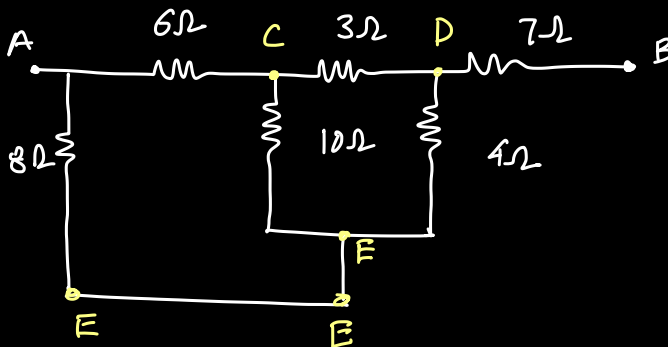


Find equivalent resistance between A & B

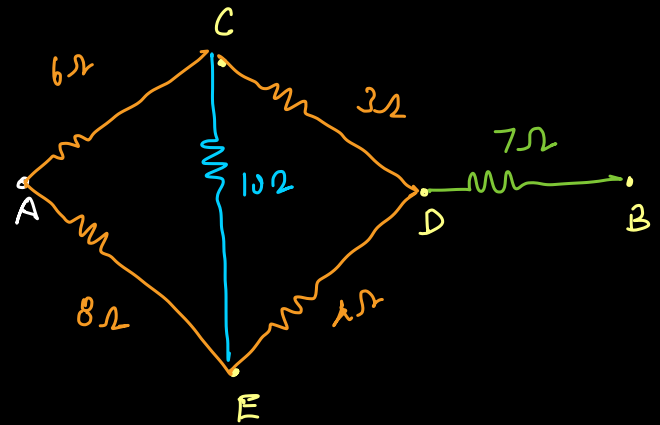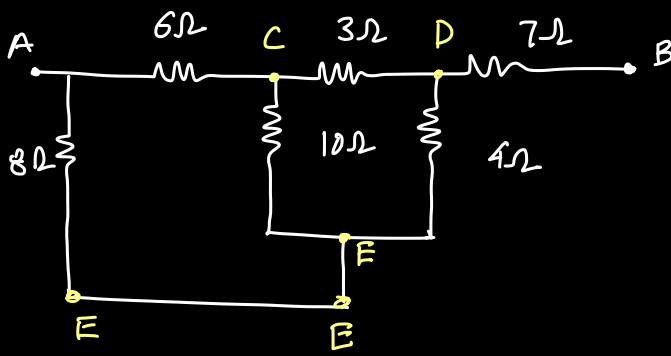

Ex

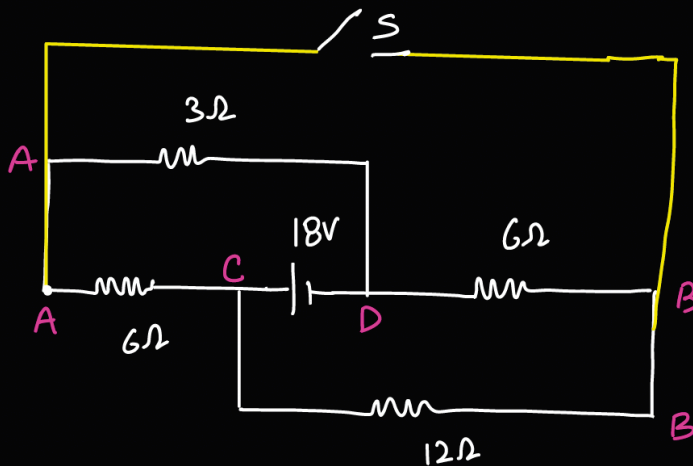

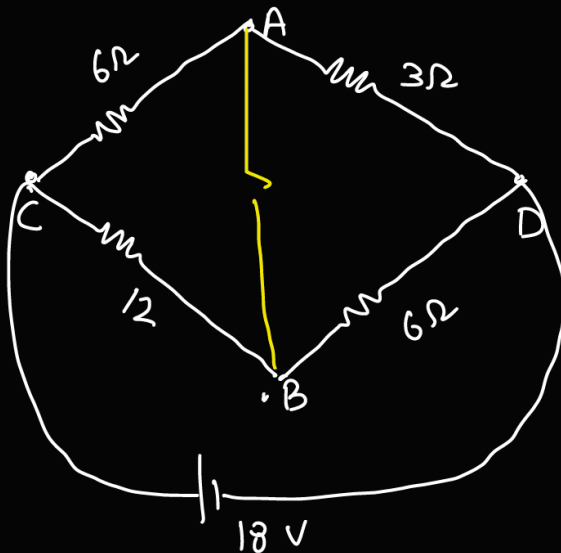Find the current through the battery when switch is
(a) open (b) closed



Balanced Wheatstone bridge
 $\Rightarrow$ It doesn't matter if switch is closed or open

$$i = \frac{18}{R_{eq}} = 3A$$

Homework

Ex1 Q 29 - 47

Ex2 Q 16 - 24, 25, 26, 29 - 45

Ex3 Q 9

Ex4 Q 5, passage 2, Q 60