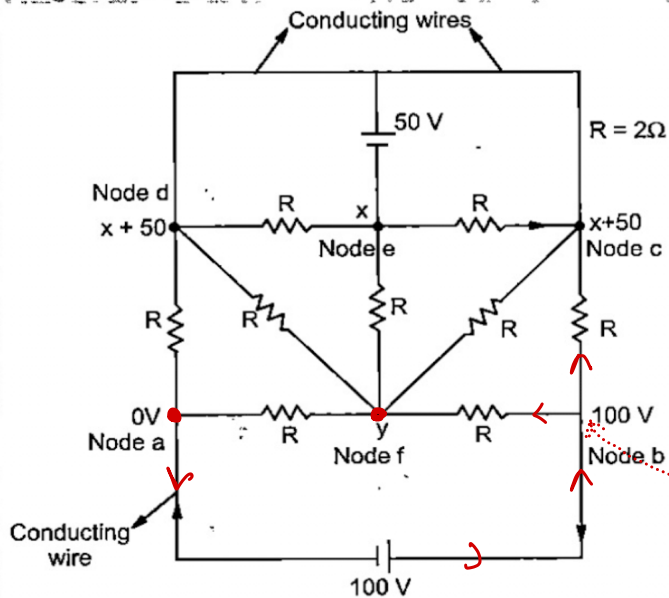


In the given circuit we wish to determine the current through resistor given in box.



This is the current from  $d \rightarrow e$  &  $e \rightarrow c$  which is same as current at  $d-b$

Node f

$$\frac{y-0}{R} + \frac{y-(x+50)}{R} \times 2 + \frac{y-x}{R} + \frac{y-100}{R} = 0$$


Node a

$$\frac{0-(x+50)}{R} + \frac{0-y}{R} + \frac{100-y}{R} + \frac{100-(x+50)}{R} = 0$$

$$x = \frac{25}{4}$$

$$y = \frac{175}{4}$$

In the circuit shown :

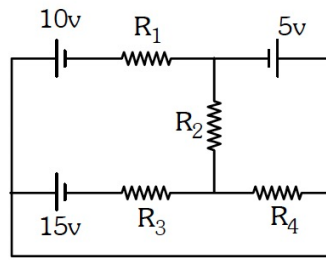


1 Current through  $R_2$  is zero if  $R_4 = 2\Omega$  and  $R_3 = 4\Omega$ . In this case :

- (A) current through  $R_3$  is 2.5 A (B) current through  $R_4$  is 3A  
(C) A and B both are correct (D) A and B both are wrong

For what ratio  $\frac{R_2}{R_4}$  current through  $R_3$  will be zero ?

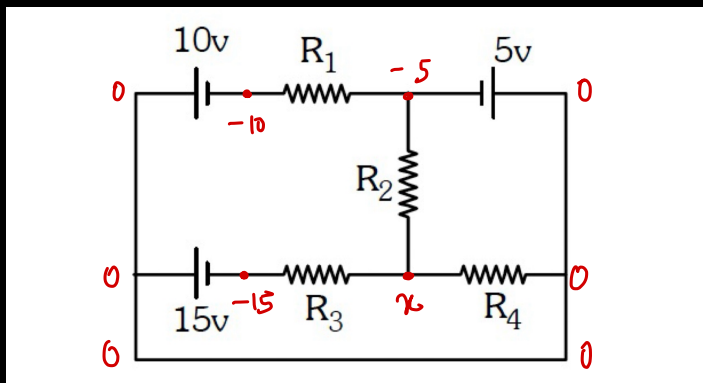- (A) 1 : 1 (B) 1 : 2 (C) 1 : 3 (D) Not possible



$$\frac{n+15}{R_3} + \frac{n-0}{R_4} + \frac{n+5}{R_2} = 0$$


For Q 2

$$n = -15$$

$$-\frac{15}{R_4} + \frac{-15+5}{R_2} = 0$$

$$\frac{R_2}{R_4} = -\frac{2}{3}$$

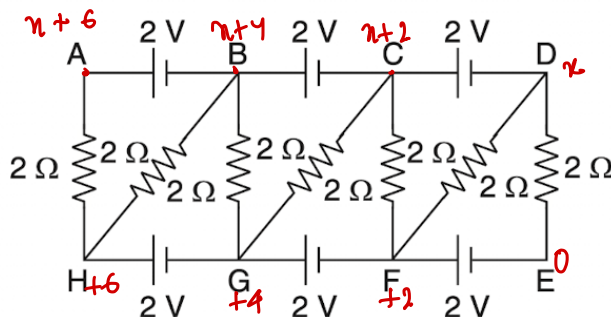In given circuit, 7 resistors  $2\Omega$  each and 6 batteries of 2 V each, are joined together.



The current through branch BG is:

- (a) 1 A (b) 0.2 A  
(c) 0.4 A (d) 0.6 A

Node D

$$\frac{n-0}{2} + \frac{n-2}{2} + \frac{n}{2} + \frac{n-2}{2} + \frac{n}{2} + \frac{n-2}{2} + \frac{n}{2} = 0$$

$$3 \left( \frac{x}{2} - 1 \right) + 4 \cdot \frac{x}{2} = 0$$


$$\frac{3x}{2} - 3 + 2x = 0$$

$$7x = 6$$

$$x = \frac{6}{7}$$

$$\text{Current in BG} = \frac{x}{2} = \frac{3}{7} \text{ A}$$


### Wheatstone bridge

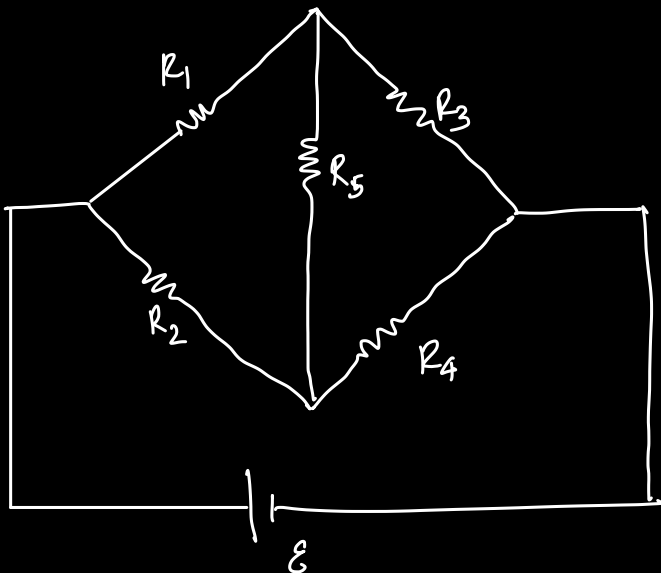

$$\text{If } \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

then current in  $R_5 = 0$

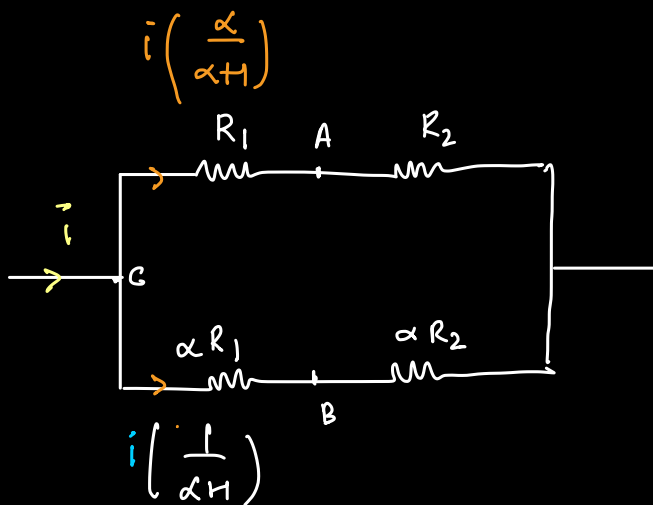At this condition the circuit is called balanced wheatstone bridge




$$V_C - V_A = i \left( \frac{\alpha}{\alpha + 1} \right) \cdot R_1$$


$$V_C - V_B = i \left( \frac{1}{\alpha + 1} \right) \cdot \alpha R_1$$

$$\Rightarrow V_A = V_B$$

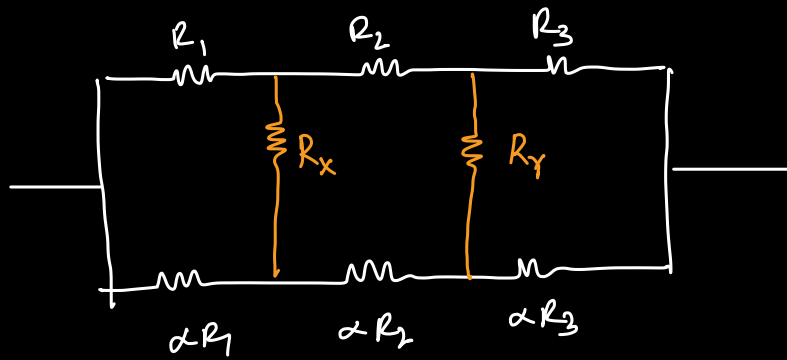
$\Rightarrow$  Any resistance connected between A & B will not carry any current



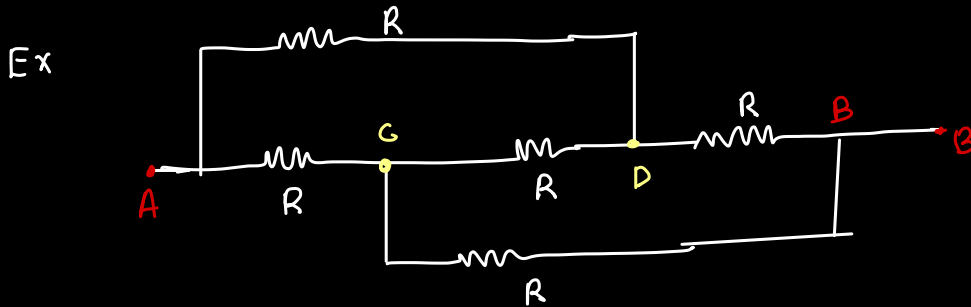current through  $R_x$  &  $R_y$  is zero




find equivalent resistance across A & B

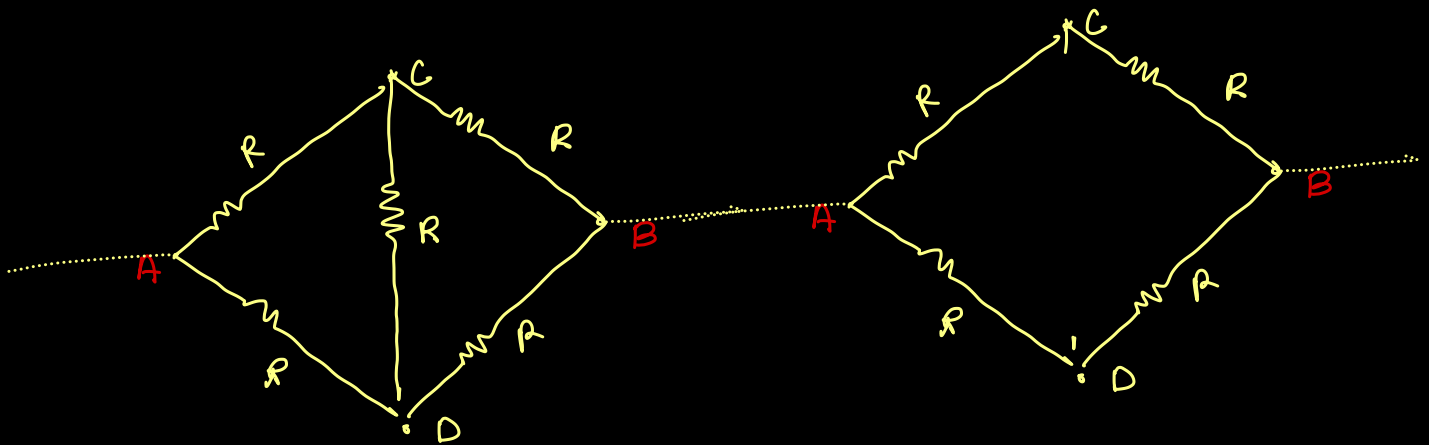

Wheatstone bridge

$$R_{AB} = R \quad \text{Ans}$$

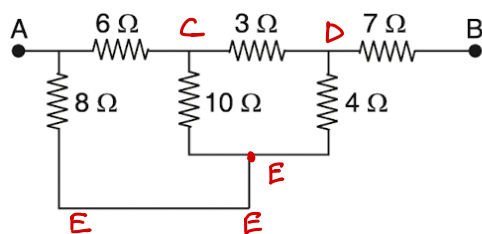The equivalent resistance between the points A and B is :




(a)  $\frac{36}{7} \Omega$


(b)  $10 \Omega$

(c)  $\frac{85}{7} \Omega$


(d) none of these

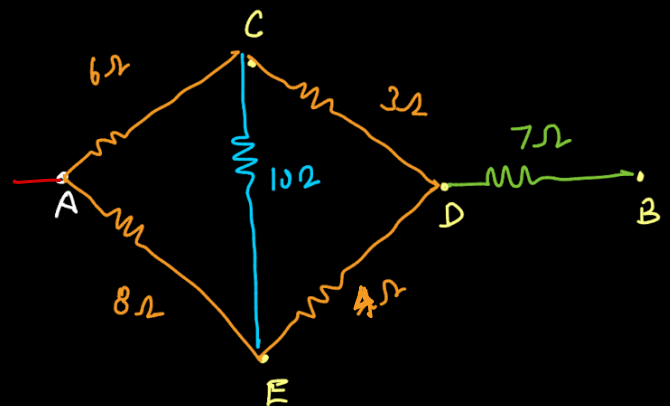

Ex

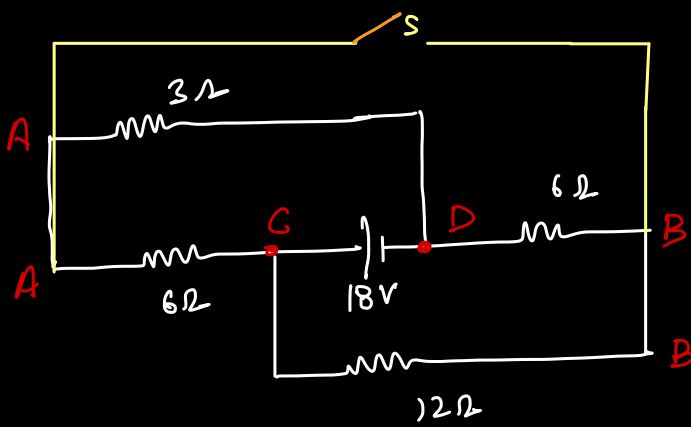

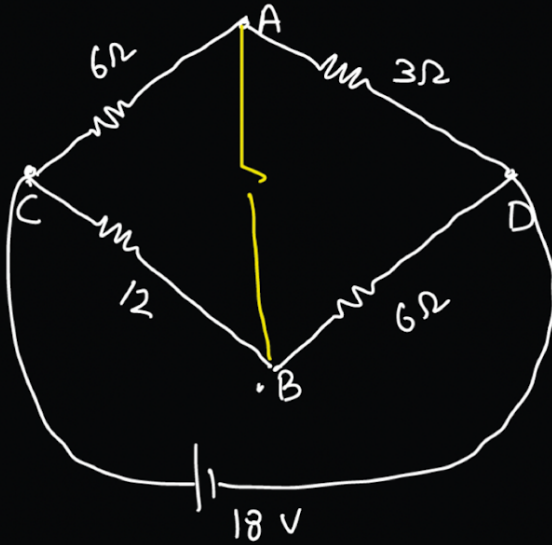Find the current through the battery if switch is  
(a) open (b) closed




Balanced Wheatstone bridge

$\Rightarrow$  It doesn't matter if switch is closed or open

$$i = \frac{18}{R_{eq}} = 3A$$

## Batteries / cells

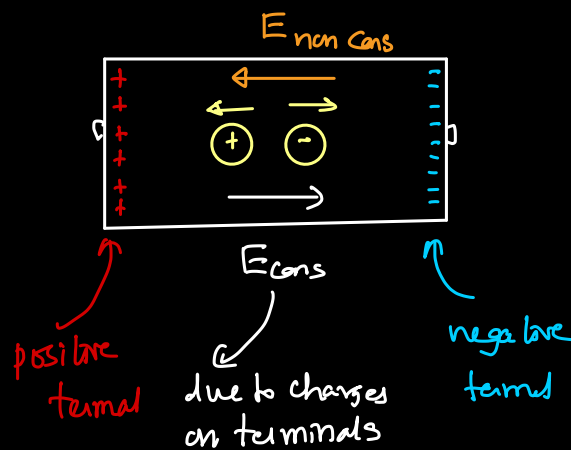

$$\mathcal{E} = \text{Emf of battery} = \int \vec{E}_{non-cons} \cdot d\vec{l}$$


Work done per unit charge by the internal non-cons electric field to take it from -ve to the terminal

$$\Delta V = \text{potential difference} = -\int \vec{E}_{\text{cons}} \cdot d\vec{l}$$


For an ideal battery

$$\Delta V = \mathcal{E}$$


Non-ideal batteries

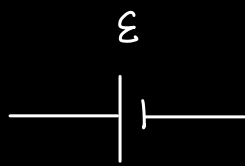

ideal battery

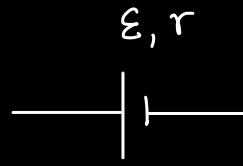

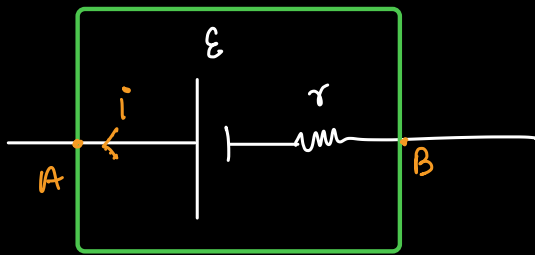non-ideal battery with  
internal resistance




$$V_A - \mathcal{E} + iR = V_B$$

$$V_A - V_B = \mathcal{E} - iR$$

Discharging

Battery is supplying  
energy to circuit

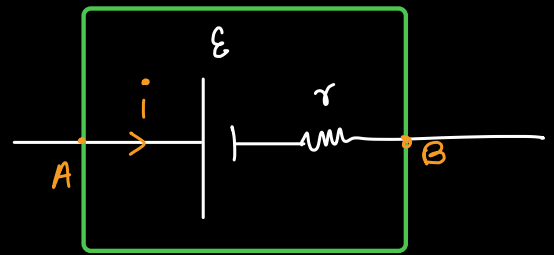


$$V_A - \mathcal{E} - iR = V_B$$

$$V_A - V_B = \mathcal{E} + iR$$

charging

Battery is absorbing  
energy from circuit

Figure shows a cell in which unit positive charge experiences a constant non electric force of 10N and a constant electric force of 8N in directions shown in the figure. The internal resistance of the cell is  $r \Omega$ . Fill  $10r$  in OMR sheet.

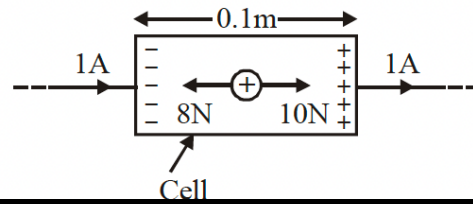

Ans: 2

$$\Delta V = \mathcal{E} - iR$$



$$\mathcal{E} - \Delta V = iR$$

$$\int \vec{E}_{non-e} \cdot d\vec{l} + \int \vec{E}_{elec} \cdot d\vec{l} = iR$$

$$10 \times 0.1 - 8 \times 0.1 = iR$$

Combination of batteries


Batteries in series

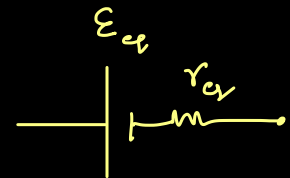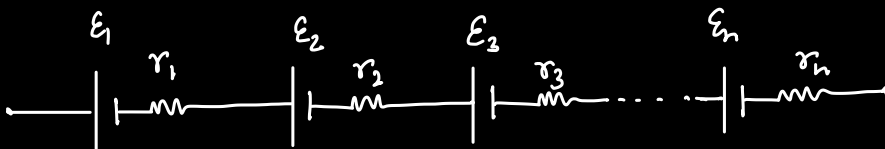

$$\mathcal{E}_q = \sum \mathcal{E}_i$$


$$r_q = \sum r_i$$

## Batteries in parallel

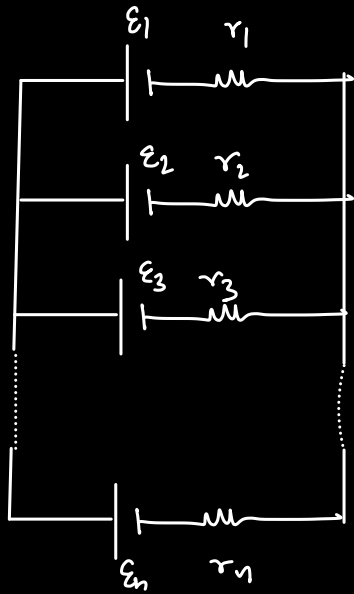


$$\mathcal{E}_q = \frac{\frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} + \dots + \frac{\mathcal{E}_n}{r_n}}{\frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}}$$
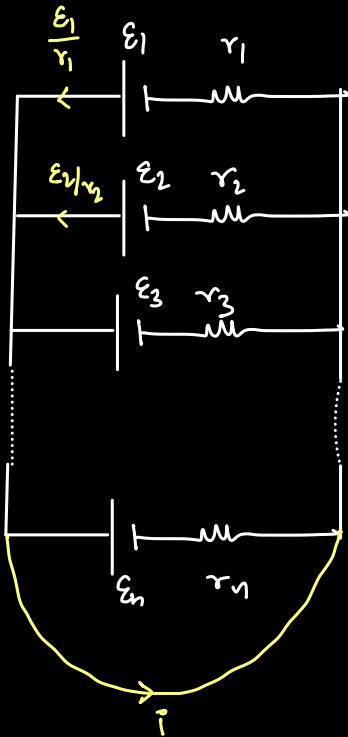
$$\frac{1}{r_q} = \frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}$$




$$i = \frac{\mathcal{E}_q}{r_q} = \frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} + \dots + \frac{\mathcal{E}_n}{r_n}$$

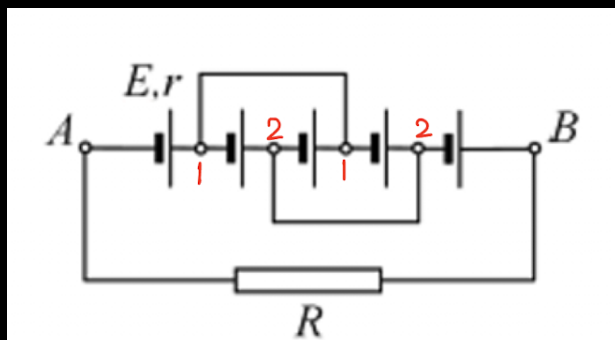
PROBLEM 12. (Moscow School of Electrical Engineering, 2017, 11) Find the current  $I$  through a resistor with a resistance  $R = 5 \text{ Ohm}$  in the circuit shown in the figure. All sources are the same and have an EMF  $E = 15 \text{ V}$  and an internal resistance  $r = 2 \text{ Ohm}$ . Neglect the resistance of the connecting wires.



Ans:  $\frac{7E}{3R+7r}$

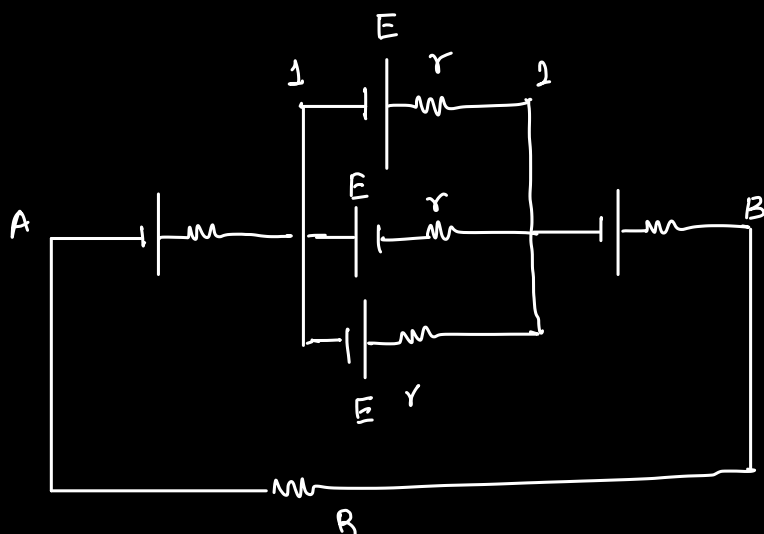

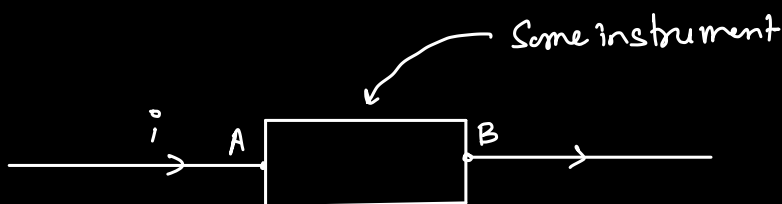
Power associated with electrical instruments



Power associated with the instrument

$$P = i \Delta V = i (V_A - V_B)$$

Thermal power dissipated in a resistor

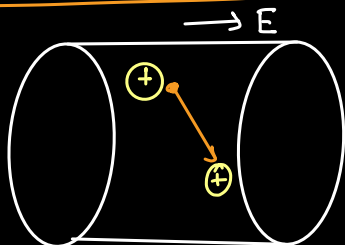

$$P = \frac{dW}{dt} = \frac{q}{dt} \Delta V = i \Delta V$$


←  $\Delta l$  →

For a resistor

$$\Delta V = iR$$

$$\begin{aligned} P &= i \Delta V \\ &= i^2 R \\ &= \frac{\Delta V^2}{R} \end{aligned}$$

## Maximum power theorem

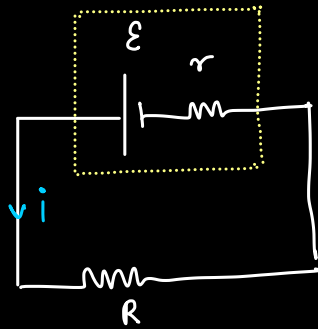

What is the condition so that rate of thermal power generated in R is maximum.



$$i = \frac{\varepsilon}{r+R}$$

$$P = i \Delta V = i^2 R = \left( \frac{\varepsilon}{r+R} \right)^2 R \longrightarrow \text{thermal power generated in } R$$

$$\frac{dP}{dR} = 0$$

$$r = R$$

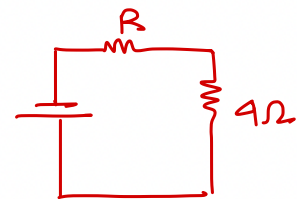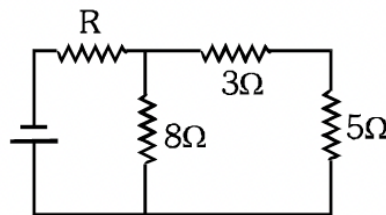The value of R so that same amount of heat is dissipated in R and rest of the circuit, is :-



✓ (A)  $4 \Omega$

(B)  $8 \Omega$


(C)  $3 \Omega$

(D)  $5 \Omega$

$$\begin{aligned} P_R &= P_{4\Omega} \\ i^2 R &= i^2 (4) \end{aligned} \quad i \longrightarrow \text{same}$$

$$R = 4$$

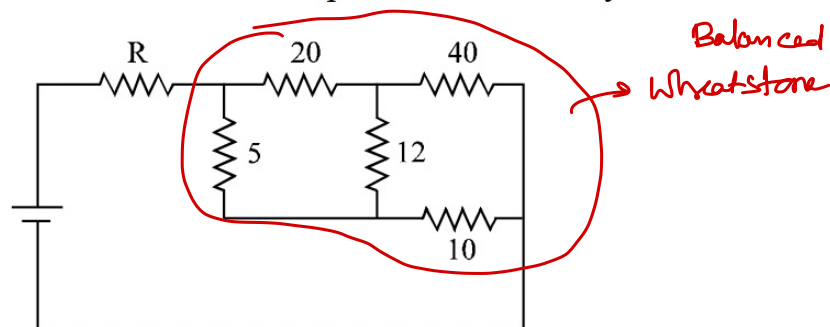What should be the value of R so that the electric power consumed by it is maximum :




(A) 12 Ω

(B) 24 Ω

(C) 6 Ω

(D) none of these

Power associated with bulbs

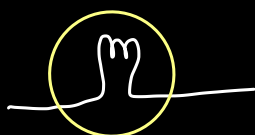

P: power rating 100 W

V: voltage rating 220 V


Imp

1. We use P & V to calculate resistance of bulb

$$R = \frac{V^2}{P}$$

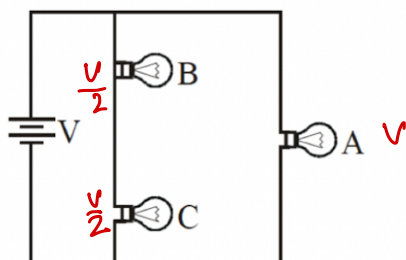2. Bulb will give an output power of P (power rating) if input voltage is V (voltage rating)

Wattage of three bulbs A, B and C rated at same voltage are  $W_A$ ,  $W_B$  and  $W_C$  respectively. Their brightness are represented by  $P_A$ ,  $P_B$  and  $P_C$ . If  $P_A = P_B = P_C$ , then correct ratio of their wattage ( $W_A : W_B : W_C$ ) is :-



(A) 1 : 2 : 3

(B) 1 : 2 : 2

(C) 1 : 4 : 4

(D) 2 : 2 : 1

$$\frac{(V/2)^2}{R_B} = \frac{(V/2)^2}{R_C} = \frac{V^2}{R_A}$$

$$W = \frac{V_0^2}{R}$$

$$W_A : W_B : W_C = \frac{1}{R_A} : \frac{1}{R_B} : \frac{1}{R_C}$$